
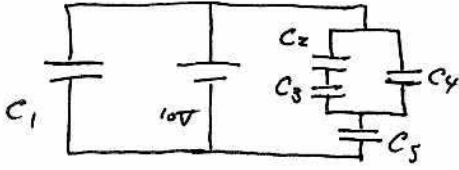


# 12

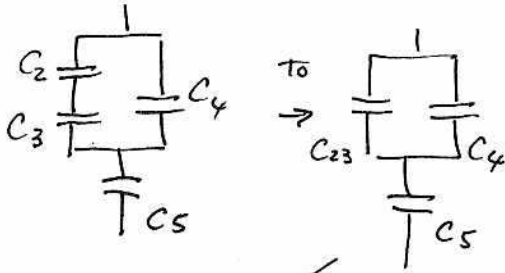


$$(a) Q_1 = CV = 10 \mu F \times 10 V = \underline{\underline{1 \times 10^{-4} C}}$$

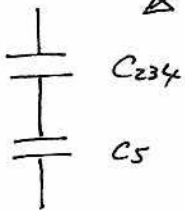
(b) Before we can calculate  $C_2$ , we need to calculate  $C_{eq}$ .



$$C_{23} = \frac{1}{\frac{1}{C_2} + \frac{1}{C_3}} = \frac{C_2 C_3}{C_2 + C_3} = \frac{10 \mu F \cdot 10 \mu F}{10 \mu F + 10 \mu F} = 5 \mu F$$


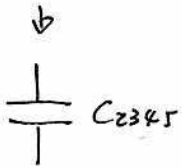
$$C_{234} = C_{23} + C_4 = 5 \mu F + 10 \mu F = 15 \mu F \text{ (parallel)}$$




$$C_{2345} = \frac{1}{\frac{1}{C_{234}} + \frac{1}{C_5}} = \frac{1}{\frac{1}{15 \mu F} + \frac{1}{10 \mu F}} = \frac{15 \mu F \cdot 10 \mu F}{15 \mu F + 10 \mu F} = \underline{\underline{6 \mu F}}$$

Hence the  $Q$  in  $C_{eq}$  is

$$Q = C_{eq} V = 6 \mu F \times 10 V = 6 \times 10^{-5} C$$

Now, going back to individual caps.

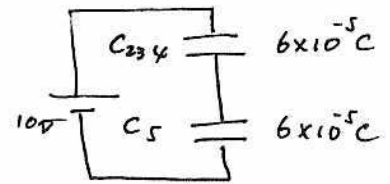
$$\text{For series, } Q_{234} = Q_5 = 6 \times 10^{-5} C$$



$\therefore V$  across  $C_{234}$  is

$$V_{(234)} = \frac{Q_{(234)}}{C_{(234)}} = \frac{6 \times 10^{-5} C}{15 \times 10^{-6} F} = 4 V$$

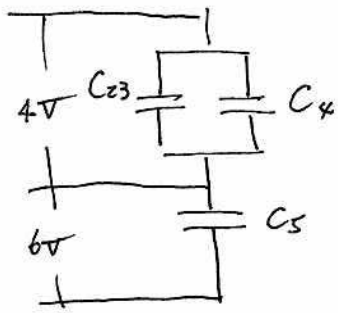(The total voltage drop across  $C_{234}$  &  $C_5$  is  $10 V$  (= the source voltage) hence  $V_5$  should be  $10 V - 4 V = 6 V$ .  
check this w/  $V = \frac{Q}{C} = \frac{Q_5}{C_5} = \frac{6 \times 10^{-5} C}{10 \times 10^{-6} F} = 6 V \checkmark$ )



$$Q_{23} = C_{23} V_{23} = 5 \times 10^{-6} \text{ F} \cdot 4 \text{ V} = \underline{\underline{2 \times 10^{-5} \text{ C}}}$$

$$(V_{23} = V_4 = 4 \text{ V})$$

Since  $Q_2 = Q_3$  (series) =  $Q_{23}$

$$\underline{\underline{Q_2 = 2 \times 10^{-5} \text{ C}}}$$

check

$$V_2 + V_3 = V_4 = 4 \text{ V}$$

$$\frac{Q_2}{C_2} + \frac{Q_3}{C_3}$$

$$= \frac{2 \times 10^{-5} \text{ C}}{10 \mu\text{F}} + \frac{2 \times 10^{-5} \text{ C}}{10 \mu\text{F}} = 2 \text{ V} + 2 \text{ V} = 4 \text{ V} \checkmark$$

Also,

$$Q_{23} + Q_4 = 6 \times 10^{-5} \text{ C}$$


$$C_{23} V_{23} + C_4 V_4$$

$$= 2 \times 10^{-5} \text{ C} + 10 \mu\text{F} \cdot 4 \text{ V}$$


$$= 2 \times 10^{-5} \text{ C} + 4 \times 10^{-5} \text{ C} = 6 \times 10^{-5} \text{ C} \checkmark$$

# 23

(a)

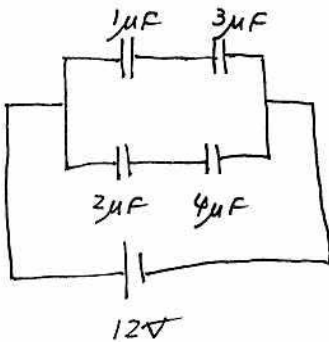

→

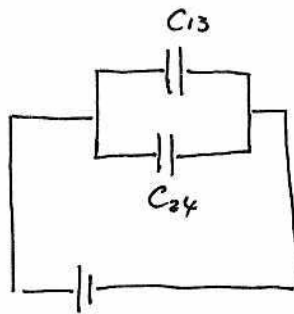



$$C_{13} = \frac{1}{\frac{1}{1} + \frac{1}{3}} = \frac{3}{4} \mu\text{F}$$

$$C_{24} = \frac{1}{\frac{1}{2} + \frac{1}{4}} = \frac{4}{3} \mu\text{F}$$

(d)


$$Q_{13} = C_{13} V_{13} = \frac{3}{4} \mu\text{F} \cdot 12 \text{ V} = \underline{\underline{9 \times 10^{-6} \text{ C}}} (= Q_1 = Q_3)$$
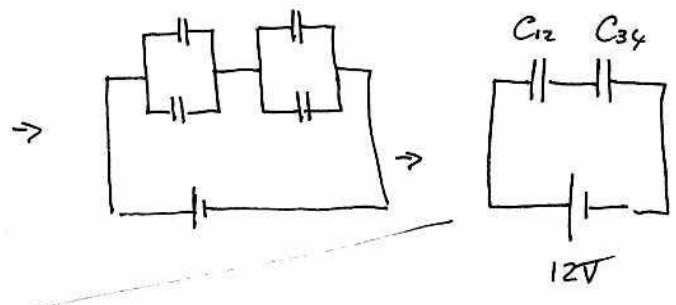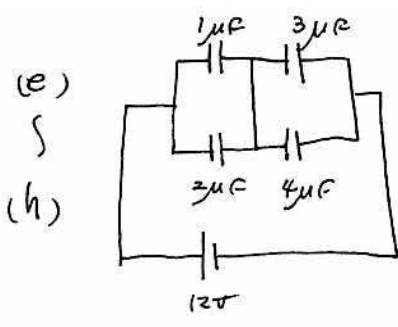
$$Q_{24} = C_{24} V_{24} = \frac{4}{3} \mu\text{F} \cdot 12 \text{ V} = \underline{\underline{16 \times 10^{-6} \text{ C}}} (= Q_2 = Q_4)$$




$$C_{12} = C_1 + C_2 = 1\mu F + 3\mu F = 3\mu F$$
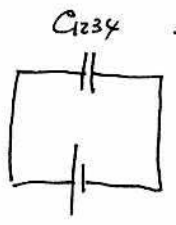
$$C_{34} = C_3 + C_4 = 3\mu F + 4\mu F = 7\mu F$$



$$C_{1234} = \frac{1}{\frac{1}{3\mu F} + \frac{1}{7\mu F}} = \frac{21}{10} \mu F = 2.1 \mu F$$
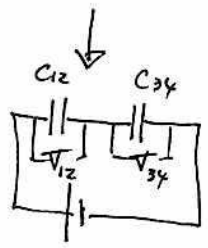
$$Q = CV = 2.1 \mu F \cdot 12V = 25.2 \mu C (= Q_{12} = Q_{34})$$



$$V_{12} = \frac{Q_{12}}{C_{12}} = \frac{25.2 \mu C}{3 \mu F} = 8.4 V$$

$$V_{34} = \frac{Q_{34}}{C_{34}} = \frac{25.2 \mu C}{7 \mu F} = 3.6 V$$

$$8.4V + 3.6V = 12V$$

(equal to the source voltage)

$$Q_1 = C_1 V_1 = C_1 V_{12} = 1 \mu F \cdot 8.4 V = 8.4 \mu C$$

$$Q_2 = C_2 V_2 = C_2 V_{12} = 3 \mu F \cdot 8.4 V = 16.8 \mu C$$

$$8.4 \mu C + 16.8 \mu C = 25.2 \mu C$$


$$Q_3 = C_3 V_3 = C_3 V_{34} = 3 \mu F \cdot 3.6 V = 10.8 \mu C$$

$$Q_4 = C_4 V_4 = C_4 V_{34} = 4 \mu F \cdot 3.6 V = 14.4 \mu C$$

$$10.8 \mu C + 14.4 \mu C = 25.2 \mu C$$

#42

Capacitance of a parallel plate

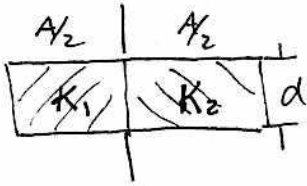

$$\begin{aligned} \text{step 1} \\ (E) \quad \oint E \cdot dA &= \frac{Q_{enc}}{\epsilon_0} \\ EA &= \frac{\sigma A}{\epsilon_0} \end{aligned}$$


$$\therefore E = \frac{\sigma}{\epsilon_0}$$

$$\text{step 2} \\ (V) \quad V = \int E \cdot dr = \int_0^d \frac{\sigma}{\epsilon_0} dr = \frac{\sigma}{\epsilon_0} d$$

$$\begin{aligned} \text{step 3} \\ (Q = CV \\ \therefore C = \frac{Q}{V}) \end{aligned}$$

$$C_0 = \frac{Q}{\frac{\sigma}{\epsilon_0} d} = \frac{\sigma A}{\frac{\sigma}{\epsilon_0} d} = \frac{A \epsilon_0}{d}$$

Applying this to the question:

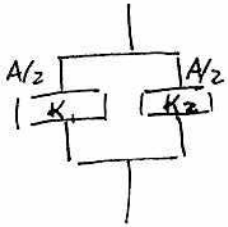

$$C_1 = K_1 \frac{(\frac{1}{2}A) \epsilon_0}{d} = K_1 \frac{A \epsilon_0}{2d}$$

$$C_2 = K_2 \frac{(\frac{1}{2}A) \epsilon_0}{d} = K_2 \frac{A \epsilon_0}{2d}$$

You can think as two parallel plate caps put them in parallel connection.

$$\therefore C_{eq} = C_1 + C_2 = K_1 \frac{A \epsilon_0}{2d} + K_2 \frac{A \epsilon_0}{2d}$$


$$= \frac{A \epsilon_0}{2d} (K_1 + K_2)$$

$$= \frac{5.56 \text{ cm}^2 \cdot \epsilon_0}{2 \cdot 5.56 \text{ mm}} (7 + 12) \quad \left( \begin{array}{l} \text{Convert them into} \\ \text{SI !!} \end{array} \right)$$

$$= \frac{5.56 \text{ cm}^2 \cdot \frac{1 \text{ m}^2}{(10^2)^2 \text{ cm}^2} \cdot \epsilon_0}{2 \cdot 5.56 \text{ mm} \cdot \frac{1 \text{ m}}{10^3 \text{ mm}}} (7 + 1)$$

$$= \underline{\underline{8.4075 \times 10^{-12} \text{ F}}}$$

#43

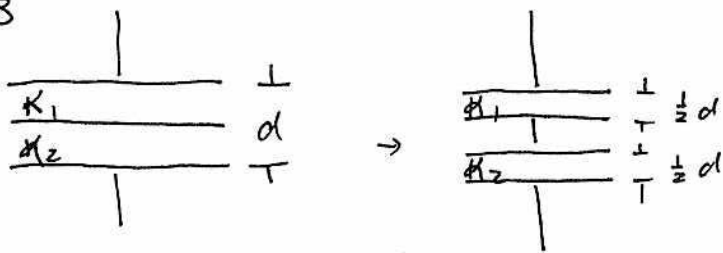

Two parallel plate caps  
connected in Series

Step 1  $E = \frac{\sigma}{\epsilon_0}$  (See #42)

Step 2  $V = \int_0^{1/2 d} E \cdot dr = \frac{\sigma}{\epsilon_0} (\frac{1}{2} d)$

Step 3  $C = \frac{Q}{V} = \frac{Q}{\frac{\sigma}{\epsilon_0} \frac{1}{2} d} = \frac{\sigma A}{\frac{\sigma d}{2 \epsilon_0}} = \frac{2 A \epsilon_0}{d}$

$\therefore C_1 = \frac{2 K_1 A \epsilon_0}{d}$  &  $C_2 = \frac{2 K_2 A \epsilon_0}{d}$

$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$

$$= \frac{\frac{2 K_1 A \epsilon_0}{d} \cdot \frac{2 K_2 A \epsilon_0}{d}}{\frac{2 K_1 A \epsilon_0}{d} + \frac{2 K_2 A \epsilon_0}{d}}$$



$$= \frac{2 K_1 A \epsilon_0 \cdot 2 K_2 A \epsilon_0}{d (2 K_1 A \epsilon_0 + 2 K_2 A \epsilon_0)}$$

$$= \frac{4 A^2 \epsilon_0^2 K_1 K_2}{2 A \epsilon_0 d (K_1 + K_2)}$$

$$= \frac{2 A \epsilon_0}{d} \frac{K_1 K_2}{K_1 + K_2} = \frac{2 \cdot 7.89 \text{ cm}^2 \cdot \epsilon_0}{4.62 \text{ mm}} \cdot \frac{11 \cdot 12}{11 + 12}$$

$$= \frac{2 \cdot 7.89 \times 10^{-6} \text{ m}^2 \cdot \epsilon_0}{4.62 \times 10^{-3} \text{ m}} \cdot \frac{11 \cdot 12}{11 + 12} = \underline{\underline{1.734819876 \times 10^{-11} \text{ F}}}$$

#44 This is a combination of #42 & 43

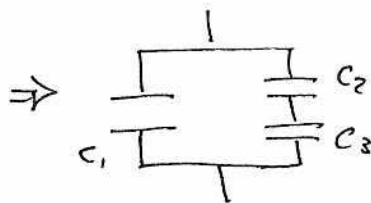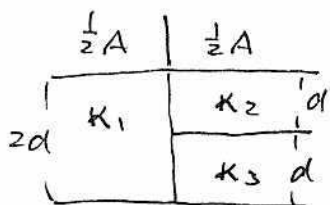

$$C_1 = \frac{\kappa_1 \cdot \frac{1}{2} A \epsilon_0}{2d}, \quad C_2 = \frac{\kappa_2 \cdot \frac{1}{2} A \epsilon_0}{d}, \quad C_3 = \frac{\kappa_3 \cdot \frac{1}{2} A \epsilon_0}{d}$$

$$= \frac{\kappa_1 A \epsilon_0}{4d}, \quad = \frac{\kappa_2 A \epsilon_0}{2d}, \quad = \frac{\kappa_3 A \epsilon_0}{2d}$$

$$C_{23} = \frac{1}{\frac{1}{C_2} + \frac{1}{C_3}} = \frac{C_2 C_3}{C_2 + C_3} = \frac{A \kappa_2 \kappa_3 \epsilon_0}{2d(\kappa_2 + \kappa_3)}$$

(series)

$$C_{123} = C_1 + C_{23}$$

(parallel)

$$= \frac{\kappa_1 A \epsilon_0}{4d} + \frac{A \kappa_2 \kappa_3 \epsilon_0}{2d(\kappa_2 + \kappa_3)}$$

$$= \frac{A \epsilon_0 (\kappa_1 (\kappa_2 + \kappa_3) + 2 \kappa_2 \kappa_3)}{4d(\kappa_2 + \kappa_3)}$$

$$= \frac{A \epsilon_0 (\kappa_1 \kappa_2 + 2 \kappa_2 \kappa_3 + \kappa_3 \kappa_1)}{4d(\kappa_2 + \kappa_3)} = \frac{10.5 \text{ cm}^2 \cdot \epsilon_0 (21 \cdot 42 + 2 \cdot 42 \cdot 58 + 58 \cdot 21)}{4 \left( \frac{2.12 \text{ mm}}{2} \right) (42 + 58)}$$

$$= \frac{10.5 \times 10^{-4} \text{ m}^2 \cdot \epsilon_0 (21 \cdot 42 + 2 \cdot 42 \cdot 58 + 58 \cdot 21)}{2 (7.12 \times 10^{-3}) (42 + 58)} = \underline{\underline{4.549670646 \times 10^{-11} \text{ F}}}$$