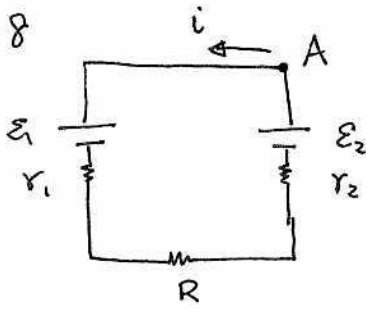


ch 27

8, 18, 27, 41, 42, 50, 55, 67, 68, 87

8



$$E_1 = 2V$$

$$E_2 = 3V$$

$$r_1 = r_2 = 3\Omega$$

$$i = 1 \times 10^{-3} A$$

Because $E_2 > E_1$, the direction of i is counter-clockwise.

(a)

Loop (starting at A)

$$-E_1 - i r_1 - i R - i r_2 + E_2 = 0$$

$$-E_1 + E_2 = i (r_1 + R + r_2)$$

$$-2 + 3 = i (3 + R + 3)$$


$$1 = i (6 + R)$$

$$\therefore R = \frac{1}{i} - 6 = \frac{1}{1 \times 10^{-3}} - 6 = \underline{\underline{994 \Omega}}$$

(b)


$$P = IV = I^2 R = (1 \times 10^{-3})^2 \cdot 994 \Omega = \underline{\underline{9.94 \times 10^{-4} W}}$$

18

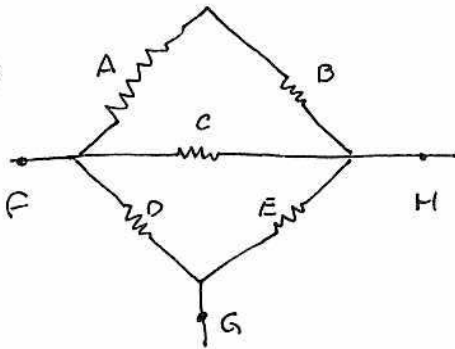


all Rs are 5Ω

(a)


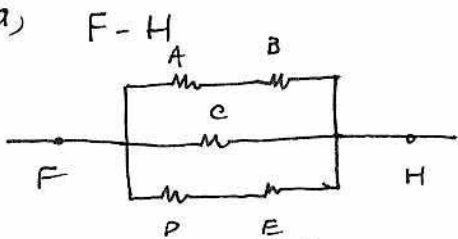


$$5 + 5 = 10 \Omega$$

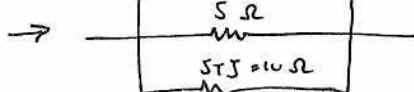


$$\rightarrow R_{eq} = \frac{1}{\frac{1}{10} + \frac{1}{5} + \frac{1}{5}} = \frac{10}{4} = \underline{\underline{2.5 \Omega}}$$


(b)

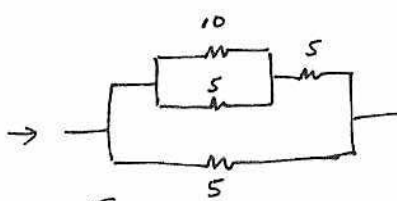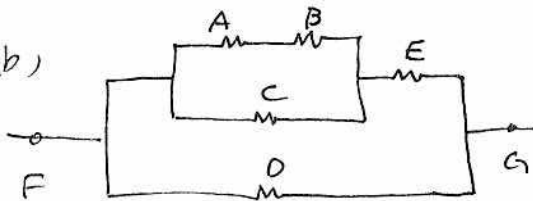

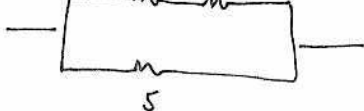
$$\frac{1}{\frac{1}{10} + \frac{1}{5}} = \frac{10}{3}$$



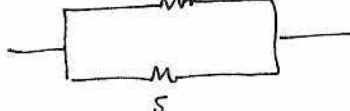
$$\frac{10}{3} + \frac{15}{3} = \frac{25}{3}$$


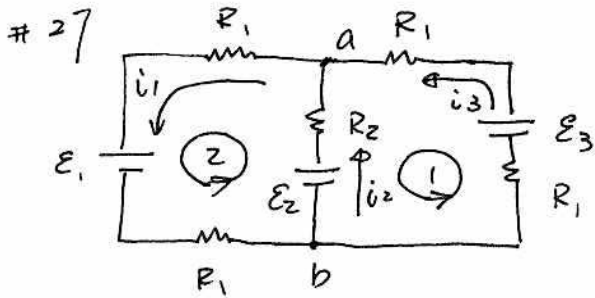
$$\rightarrow R_{eq} = \frac{1}{\frac{3}{25} + \frac{1}{5}} = \underline{\underline{\frac{25}{8} \Omega}}$$


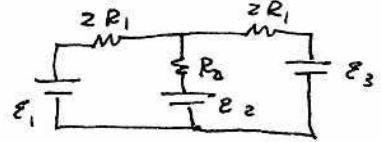
$$\begin{aligned} \mathcal{E}_1 &= 2\text{V} \\ \mathcal{E}_2 &= \mathcal{E}_3 = 4\text{V} \\ R_1 &= 1\Omega \\ R_2 &= 2\Omega \end{aligned}$$



You can solve this by reducing first to . But I will do the harder way to show it still works.

Junction Rule (at a)

$$i_2 + i_3 = i_1 \quad \text{--- (1)}$$

Loop 1 (at a)

$$i_2 R_2 - \mathcal{E}_2 - i_3 R_1 + \mathcal{E}_3 - i_3 R_1 = 0$$

$$2i_2 - 4 - i_3 + 4 - i_3 = 0$$

$$\therefore 2i_2 - 2i_3 = 0$$

$$\therefore i_2 = i_3 \quad \text{--- (2)}$$

Loop 2 (at a)

$$-i_1 R_1 - \mathcal{E}_1 - i_1 R_1 + \mathcal{E}_2 - i_2 R_2 = 0$$

$$i_1 - 2 - i_1 + 4 - 2i_2 = 0$$

$$-2i_1 + 2 - 2i_2 = 0$$

$$\therefore -i_1 + 1 - i_2 = 0$$

$$i_2 = 1 - i_1 \quad \text{--- (3)}$$

$$\textcircled{1} \leftarrow \textcircled{2} \leftarrow \textcircled{3}$$

$$(1 - i_1) + (1 - i_1) = i_1$$

$$2 - 2i_1 = i_1$$

$$3i_1 = 2$$

(a) & (b)

$$\therefore i_1 = \frac{2}{3} \text{ amp} \quad \text{--- (1)'} \downarrow$$

(c) & (d)

$$\textcircled{3} \leftarrow \textcircled{1}'$$

$$i_2 = 1 - \frac{2}{3} \text{ ap}$$


$$= \frac{1}{3} \text{ ap} \quad \text{--- (2)'} \downarrow$$

(e) & (f)

$$\textcircled{2} \leftarrow \textcircled{2}'$$

$$i_3 = \frac{1}{3} \text{ ap} \quad \uparrow$$

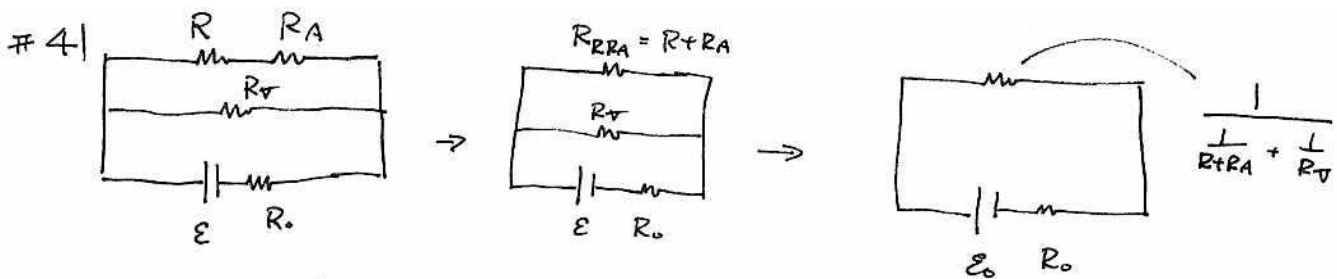(g) $V_a - V_b = i_2 R_2 - \mathcal{E}_2 = \frac{1}{3} \cdot 2 - 4 = \underline{\underline{-\frac{10}{3} \text{V}}}$



(a) $R_T = \frac{R_V(R+R_A)}{R+R_A+R_V} + R_0 = \frac{300(85+3)}{300+85+3} + 100 = 168.0412371 \Omega$

$i_T = \frac{V_T}{R_T} = \frac{12V}{168.041} = \underline{\underline{7.141104295 \times 10^{-2} \text{ amp}}}$

$V\left(\frac{1}{\frac{1}{R+R_A} + \frac{1}{R_V}}\right) = i_T R \frac{1}{\frac{1}{R+R_A} + \frac{1}{R_V}}$


$= 7.14 \dots \frac{R_V(R+R_A)}{R+R_A+R_V} = \underline{\underline{4.8558895706 V}}$

$\therefore i(\text{through } \textcircled{A}) = \frac{V}{R} = \frac{4.855 \dots}{85+3} = \underline{\underline{5.521472393 \times 10^{-2} \text{ ap}}}$

(b) $V = V\left(\frac{1}{\frac{1}{R+R_A} + \frac{1}{R_V}}\right) = \underline{\underline{4.8558895706 V}}$

(c) $R' = \frac{V'}{i} = \frac{4.85 \dots}{5.52 \dots} = \underline{\underline{88 \Omega}}$

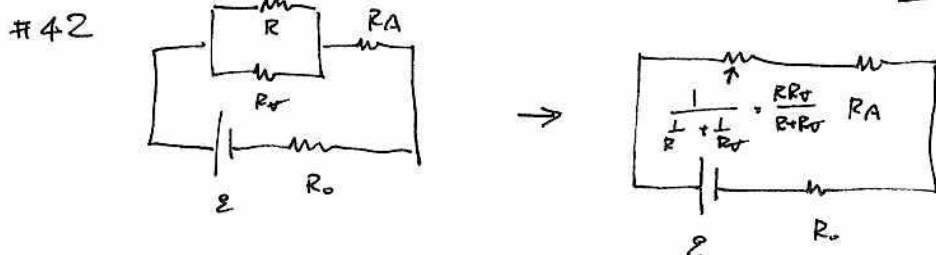(d) If $R_A \downarrow$, $R_T \downarrow$, $i_T \uparrow$, $V \downarrow$, $\therefore R' = \frac{V}{i} \downarrow$



(a) $R_T = \frac{R R_V}{R+R_V} + R_A + R_0 = \frac{85 \cdot 300}{85+300} + 3 + 100 = 1.69 \times 10^2 \Omega$


$i = \frac{V}{R_T} = \frac{12}{1.69 \times 10^2} = \underline{\underline{7.09 \times 10^{-2} \text{ amp}}}$

(b) $V = i R_{eq} = 7.09 \times 10^{-2} \text{ ap} \cdot \frac{R R_V}{R+R_V} = 4.696492978 V$

(c) $R' = \frac{V}{i} = \frac{4.696 \dots}{7.09 \times 10^{-2}} = 66.23376623 \Omega$ (way off for real R because R_V is too small)

(d) $R_V \uparrow$, $R_T \uparrow$, $i \downarrow$, $R' = \left(\frac{V}{i}\right) \uparrow$

52

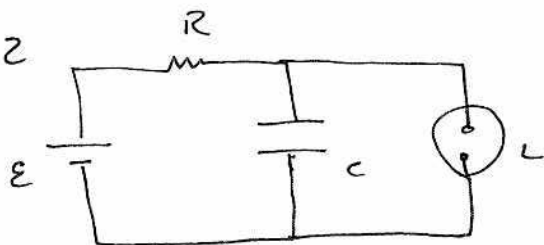

$$C = 0.15 \mu\text{F}$$

$$\mathcal{E} = 95\text{V}$$

$$V_L = 72\text{V}$$

$$2 \text{ flashes/sec} \Rightarrow t = 0.5 \text{ sec}$$

$$V_C = \mathcal{E} (1 - e^{-\frac{t}{RC}}) \quad \left[\text{you should be able to derive this} \right]$$

$$\frac{V_C}{\mathcal{E}} = (1 - e^{-\frac{t}{RC}})$$

$$e^{-\frac{t}{RC}} = 1 - \frac{V_C}{\mathcal{E}}$$


$$-\frac{t}{RC} = \ln\left(1 - \frac{V_C}{\mathcal{E}}\right)$$

$$R = \frac{-t}{C \ln\left(1 - \frac{V_C}{\mathcal{E}}\right)}$$

$$\left(\begin{array}{l} \text{at } t=0, V_C = 0 \\ t = 0.5 \text{ sec}, V_C = 72\text{V} \end{array} \right)$$

$$= \frac{-0.5}{0.15 \times 10^{-6} \left(1 - \frac{72}{95}\right)} = \underline{\underline{2350094.506 \Omega}} \quad (2.35 \times 10^6 \Omega)$$

55

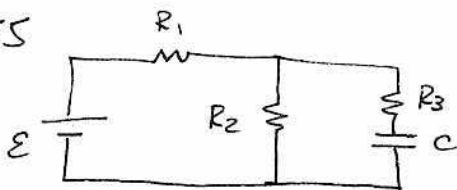


$$\mathcal{E} = 1200\text{V}$$

$$C = 6.5 \times 10^{-6} \text{ F}$$

$$R_1 = R_2 = R_3 = 0.73 \times 10^6 \Omega$$

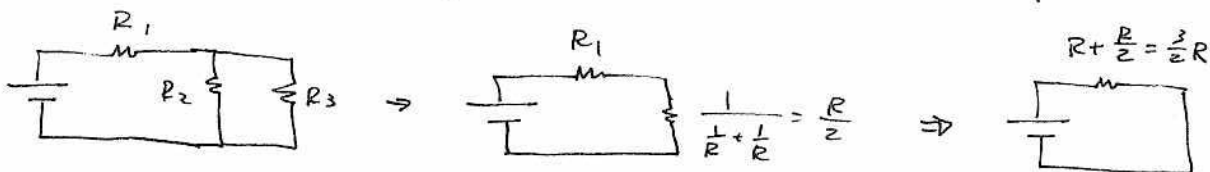(a), (b), & (c) when $t=0$, C is considered "short circuited".




$$\therefore i = \frac{V}{R_{\text{eq}}} = \frac{1200}{\frac{3}{2}R} = \underline{\underline{1.095890411 \times 10^{-3} \text{ ap}}} (= i_1)$$

Because $R_2 = R_3$, the current will split half & half

$$i_2 = i_3 = \underline{\underline{5.479452055 \times 10^{-4} \text{ ap}}} (= i_2 = i_3)$$

(d), (e), & (f) when $t=\infty$, $i_3 = 0$ because C is fully charged.

So, the circuit is considered as:

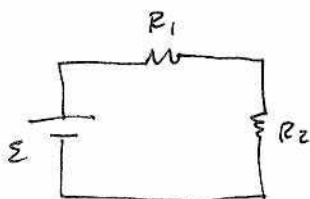


$$R_{\text{eq}} = R_1 + R_2$$

$$i = \frac{V}{R_{\text{eq}}} = \underline{\underline{8.21978082 \times 10^{-4} \text{ ap}}} (= i_1 = i_3)$$

(g), (h), & (i)

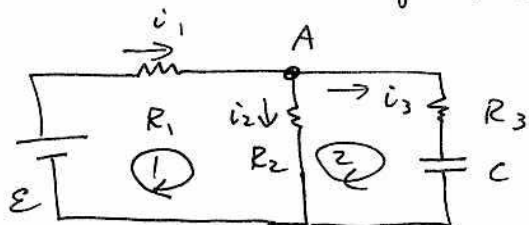You can calculate $V_2(t=0)$ by $i(t=0)R_2$ ($= 400V$) and $V_2(t=\infty)$ by $i(t=\infty)R_2$ ($= 600V$). But I want to show another way so that we can calculate i_2 as a fun of time (which you should be able to do)



Junction Rule (at A)

$$i_1 = i_2 + i_3 \quad \text{--- (1)}$$

$$i_3 = \frac{dq}{dt} \quad \left(\begin{array}{l} \text{the current that goes} \\ \text{a capacitor is } \frac{dq}{dt} \end{array} \right)$$

Loop 1 (at A)

$$-i_2 R_2 + E - i_1 R_1 = 0 \quad \text{--- (2)}$$

Loop 2 (at A)

$$-i_3 R - \frac{q}{C} + i_2 R = 0 \quad \text{--- (3)}$$

$$\text{(2)} \leftarrow \text{(1)}$$

$$-i_2 R + E - (i_2 + i_3) R = 0$$

$$-i_2 R + E - i_2 R - i_3 R = 0$$

$$-2i_2 R - i_3 R + E = 0$$

$$2i_2 R = E - i_3 R$$

$$\therefore i_2 = \frac{E - i_3 R}{2R} \quad \text{--- (2)'}$$

$$\text{(3)} \leftarrow \text{(2)'}$$

$$-i_3 R - \frac{q}{C} + \left(\frac{E - i_3 R}{2R} \right) R = 0$$

$$-i_3 R - \frac{q}{C} + \frac{E}{2} - \frac{i_3 R}{2} = 0$$

$$-\frac{3}{2} i_3 R - \frac{q}{C} + \frac{E}{2} = 0 \quad \left[\text{We want solve for } i_3 \text{ since } i_3 = \frac{dq}{dt} \right]$$

$$\therefore i_3 = \frac{2}{3R} \left(-\frac{q}{C} + \frac{E}{2} \right) = \frac{2}{3R} \left(\frac{-2q + EC}{2C} \right)$$

$$= \frac{-1}{3RC} (2q - EC)$$

$$= \frac{-2}{3RC} \left(q - \frac{EC}{2} \right) = \frac{dq}{dt}$$

$$\int \frac{-2}{3RC} dt = \int \frac{1}{q - \frac{\epsilon C}{2}} dq$$

$$e^{\frac{-2t}{3RC}} = e^{\ln(q - \frac{\epsilon C}{2})} + \alpha$$

$$e^{\frac{-2t}{3RC}} = (q - \frac{\epsilon C}{2}) \alpha'$$

when $t=0$, $q=0$

$$\therefore 1 = -\frac{\epsilon C}{2} \alpha'$$

$$\therefore \alpha' = -\frac{2}{\epsilon C}$$

So the fun is

$$e^{\frac{-2t}{3RC}} = (q - \frac{\epsilon C}{2}) (-\frac{2}{\epsilon C})$$

$$\therefore q = \frac{\epsilon C}{2} (1 - e^{\frac{-2t}{3RC}})$$

$$\text{So, } i_3 = \frac{dq}{dt} = \frac{\epsilon C}{2} \frac{2}{3RC} e^{\frac{-2t}{3RC}} = \frac{\epsilon}{3R} e^{\frac{-2t}{3RC}} \quad \text{--- (3)'}$$

$$\text{(2)'} \longleftarrow \text{--- (3)'}$$

$$i_2 = \frac{\epsilon - (\frac{\epsilon}{3R} e^{\frac{-2t}{3RC}}) R}{2R} = \frac{\epsilon}{2R} (1 - \frac{1}{3} e^{\frac{-2t}{3RC}})$$

$$\therefore V_{(R_2)} = i_2 R_2$$

$$= \frac{\epsilon}{2} (1 - \frac{1}{3} e^{\frac{-2t}{3RC}})$$

$$\text{When } t=0 \quad V_{(R_2)} = \frac{\epsilon}{2} (1 - \frac{1}{3} e^0) = \frac{1}{3} \epsilon = 400V$$

$$t=\infty \quad V_{(R_2)} = \frac{\epsilon}{2} (1 - \frac{1}{3} e^{-\infty}) = \frac{1}{2} \epsilon = 600V \quad \left. \vphantom{\begin{matrix} t=0 \\ t=\infty \end{matrix}} \right\} \text{they match !!}$$




(Extra) $\tau_c = \frac{3}{2} RC$ in this case and $\infty \sim 6RC$

$$\begin{aligned} \text{So } \infty &= 6RC = 6 \cdot \frac{3}{2} RC \\ &= 9 (0.73 \times 10^6) (6.5 \times 10^6) \\ &= \underline{\underline{42.705 \text{ sec}}} \end{aligned}$$

So Physically, $t \geq 42.705 \text{ sec}$ is ∞ for this circuit.

#89

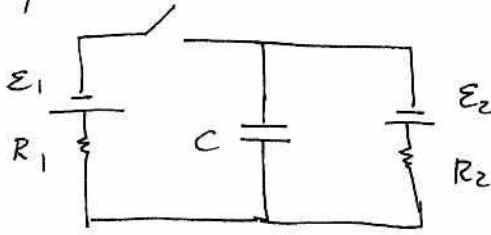

$$C = 10 \mu\text{F}$$


$$E_1 = 1\text{V}$$

$$E_2 = 3\text{V}$$

$$R_1 = 0.2 \Omega$$

$$R_2 = 0.4 \Omega$$

First condition

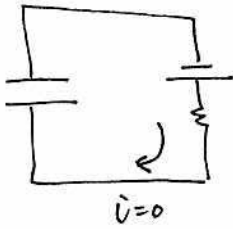


Since the cap is fully charged, $i = 0$
and $V_C = E$

$$\therefore Q_i = CV$$

$$= 10 \mu\text{F} \cdot 3\text{V} = \underline{\underline{30 \mu\text{C}}}$$

Second condition

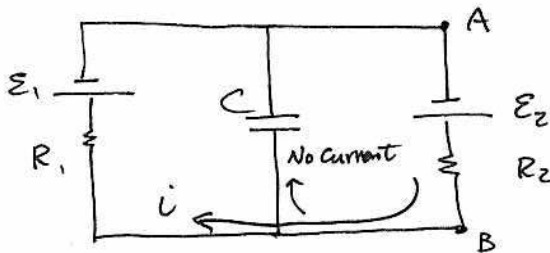

Loop 1 at A

$$E_2 - iR_2 - iR_1 - E_1 = 0$$

$$E_2 - E_1 - i(R_1 + R_2) = 0$$

$$3 - 1 - i(0.2 + 0.4) = 0$$

$$2 - i(0.6) = 0$$

$$\therefore i = \frac{2}{0.6} = \frac{10}{3} \text{ amp}$$

$$V_C = V_{AB} = E_2 - iR_2$$

$$= 3 - \frac{10}{3} \cdot 0.4 = \underline{\underline{\frac{5}{3} \text{V}}}$$

$$\therefore Q_f = CV$$


$$= 10 \mu\text{F} \cdot \frac{5}{3} \text{V} = \underline{\underline{\frac{50}{3} \mu\text{C}}}$$

$$\Delta Q = Q_f - Q_i = \frac{50}{3} \mu\text{C} - 30 \mu\text{C}$$

$$= \frac{50}{3} \mu\text{C} - \frac{90}{3} \mu\text{C}$$

$$= \underline{\underline{-\frac{40}{3} \mu\text{C}}}$$

#67

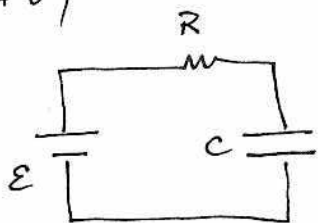

a) Energy stored in the cap. when it is fully charged

$$\begin{aligned}
 U &= \frac{1}{2} C V^2 \\
 &= \frac{1}{2} \frac{q}{V} \cdot V^2 \\
 &= \frac{1}{2} q V
 \end{aligned}$$

$$q = C V \rightarrow C = \frac{q}{V}$$

While the charge "q" is moving to the cap., the work or energy released by the battery is

$$W = q V$$

Hence a half of work done by the battery is stored in the cap. (the other half? it was used up by the resistor)

b)

$$V = V_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

(I started w/ this, but you should be able to derive this w/o any trouble)

since

$$P = I^2 R \quad \& \quad W = \int P \cdot dt$$

$$W = \int I^2 R \cdot dt$$

We need to get $I(t)$.

$$q = C V = C V_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

$$\therefore i(t) = \frac{dq}{dt} = \frac{d(C V_0 (1 - e^{-\frac{t}{RC}}))}{dt} = \frac{V_0}{R} e^{-\frac{t}{RC}}$$

$$\therefore W = \int i^2 R \cdot dt$$


$$= \int \left(\frac{V_0}{R} e^{-\frac{t}{RC}}\right)^2 \cdot R \cdot dt$$

$$= \int \frac{V_0^2}{R} e^{-\frac{2t}{RC}} \cdot dt$$

$$= \frac{V_0^2}{R} \left(-\frac{RC}{2}\right) e^{-\frac{2t}{RC}} \Big|_0^\infty$$

$$= \frac{V_0^2 C}{2} = \frac{1}{2} C V_0^2 \quad \dots \text{the same result.}$$

#68

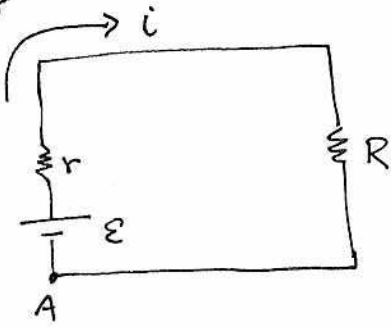

starting at A

$$\varepsilon - i r - i R = 0$$

$$V = i(r + R)$$

$$i = \frac{V}{r + R} \quad \text{--- (1)}$$

$$P = iV = i^2 R \quad \text{--- (2)}$$

$$\text{(2)} \leftarrow \text{(1)}$$

$$P = \left(\frac{V}{r + R} \right)^2 R \quad \text{--- (2')}$$

$$= V^2 \cdot \frac{R}{(r + R)^2}$$

To maximize P , set $\frac{dP}{dR} = 0$ (Because V & r are const. only R is a factor to decide P)

$$\begin{aligned} \frac{dP}{dR} &= \frac{d\left(V^2 \cdot \frac{R}{(r+R)^2}\right)}{dR} = V^2 \left(\frac{1}{(r+R)^2} - \frac{2R}{(r+R)^3} \right) \\ &= V^2 \left(\frac{(r+R) - 2R}{(r+R)^3} \right) \\ &= V^2 \left(\frac{r - R}{(r+R)^3} \right) = 0 \end{aligned}$$

$$\therefore r - R = 0 \quad \text{or} \quad \underline{\underline{R = r}} \quad \text{--- (2'')}$$

$$\text{(2'')} \leftarrow \text{(2)'}$$

$$P = \left(\frac{V}{r + r} \right)^2 \cdot r$$

$$= \left(\frac{V}{2r} \right)^2 \cdot r$$

$$= \frac{V^2}{4r^2} \cdot r$$

$$= \underline{\underline{\frac{V^2}{4r}}}$$