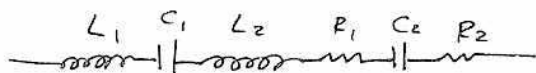


ch. 31 # 8, 13, 44, 46, 49, 56, 57, 59, 98

8



Loop law



$$+L_1 \frac{di}{dt} + \frac{q_1}{C_1} + iR_1 + \frac{q_2}{C_2} + iR_2 + \dots$$

$$(L_1 + L_2 + \dots) \frac{di}{dt} + \left(\frac{q_1}{C_1} + \frac{q_2}{C_2} + \dots \right) + i(R_1 + R_2 + \dots)$$

$q_1 = q_2 = \dots$ for series

$$\underline{L_{eq} \frac{di}{dt} + \frac{q}{C_{eq}} + iR_{eq}}$$

13.

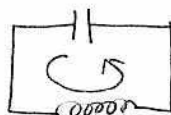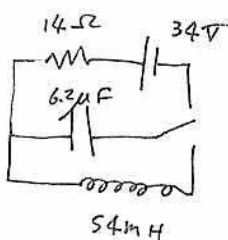

a)

loop

$$-\frac{q}{C} - L \frac{di}{dt} = 0$$

$$\frac{1}{C} q + L \frac{di}{dt} = 0$$

$$i = \frac{dq}{dt} = \dot{q}$$

$$\therefore \frac{di}{dt} = \frac{d^2q}{dt^2} = \ddot{q}$$

$$\frac{1}{C} q + L \ddot{q} = 0 \quad (\text{This is a simple harmonic oscillation!})$$

Let

$$q = A \cos(\omega t + \phi)$$

$$\dot{q} = -A\omega \sin(\omega t + \phi)$$

$$\ddot{q} = -A\omega^2 \cos(\omega t + \phi)$$

$$\frac{1}{C} A \cos(\omega t + \phi) + L (-A\omega^2 \cos(\omega t + \phi)) = 0$$

$$A \cos(\omega t + \phi) \left(\frac{1}{C} - L\omega^2 \right) = 0$$

$$\therefore \frac{1}{C} - L\omega^2 = 0$$

$$\omega = \sqrt{\frac{1}{LC}}$$


$$\nu = \frac{\omega}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 2.750599799 \times 10^2 \text{ Hz}$$

b) when $t=0$, q is max ($= CV = 6.2 \times 10^{-6} \cdot 34$)

$$q = CV = A \cos(\omega t + \phi) = 6.2 \times 10^{-6} \cdot 34 = 2.108 \times 10^{-4} \text{ C}$$

$$\therefore \dot{q} = \underbrace{-\omega A}_{\text{Amp. for } \dot{q}} \sin(\omega t + \phi) = \underline{\underline{0.3643156954 \text{ amp}}}$$

44

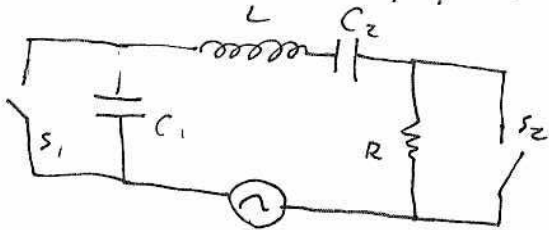


$$E_{\text{max}} = 12 \text{ V}$$

$$\nu = 60 \text{ Hz}$$

$$C_1 = C_2$$

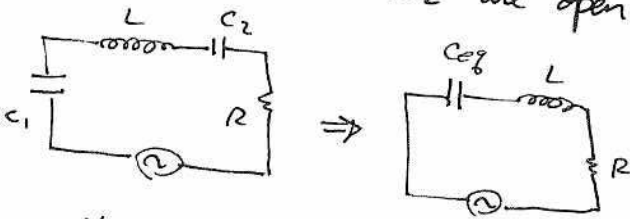Case I: when S_1 & S_2 are open, i leads ε by 30°



$$C_{\text{eq}} = \frac{1}{\frac{1}{C} + \frac{1}{C}} = \frac{1}{2} C$$


$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C_{\text{eq}}} = \frac{2}{\omega C}$$

$$\phi_1 = \tan^{-1} \frac{X_L - X_C}{R} = \tan^{-1} \frac{\omega L - \frac{2}{\omega C}}{R} = -30.9^\circ$$

$$\therefore \frac{\omega L - \frac{2}{\omega C}}{R} = \tan \phi_1 \quad \text{--- (1)}$$

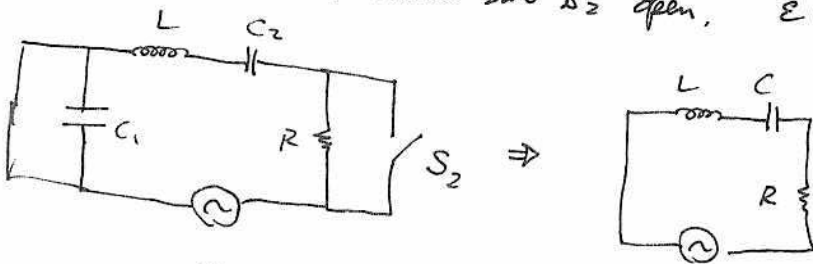Case 2: when S_1 closed but S_2 open, ε leads i by 15°




$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$


$$\phi_2 = \tan^{-1} \frac{X_L - X_C}{R} = \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R} = 15.0^\circ$$

$$\therefore \frac{\omega L - \frac{1}{\omega C}}{R} = \tan \phi_2 \quad \text{--- (2)}$$

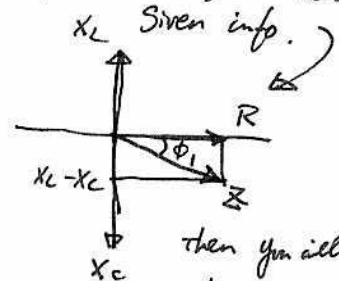You should be able to construct an impedance diagram from the given info.



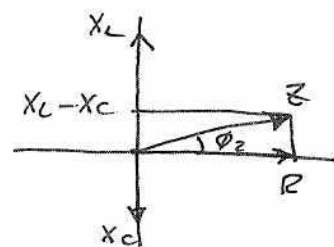
then you will see why $\phi_1 = -30.9^\circ$




$$Z = \sqrt{(X_L - X_C)^2}$$

$$= (X_L - X_C)$$
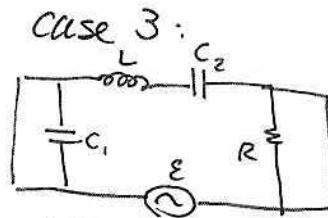
$$\frac{\mathcal{E}}{i} = Z = X_L - X_C = 447 \text{ m}\Omega$$



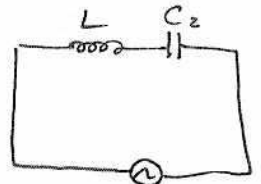Both switches closed,
 $i = 447 \text{ mA}$



$$\frac{\mathcal{E}}{i} = \omega L - \frac{1}{\omega C}$$

$$\omega L = \frac{\mathcal{E}}{i} + \frac{1}{\omega C}$$

$$L = \frac{\frac{\mathcal{E}}{i} + \frac{1}{\omega C}}{\omega} \quad \text{--- (2)}$$

(2) ← (3)

$$\frac{\omega \left(\frac{\mathcal{E}}{i} + \frac{1}{\omega C} \right) - \frac{1}{\omega C}}{R} = \tan 15^\circ$$

$$\frac{\frac{\mathcal{E}}{i} + \frac{1}{\omega C} - \frac{1}{\omega C}}{R} = \tan 15^\circ$$

$$\therefore R = \frac{\frac{\mathcal{E}}{i}}{\tan 15^\circ} = \frac{\frac{12}{447 \times 10^{-3}}}{\tan 15^\circ} = \underline{\underline{100.1892834 \Omega}} \quad \text{--- (2')}$$

(1) ← (3) ≠ (2)'

$$\frac{\omega \left(\frac{\mathcal{E}}{i} + \frac{1}{\omega C} \right) - \frac{2}{\omega C}}{R} = \tan(-30.9^\circ)$$

$$\frac{\frac{\mathcal{E}}{i} + \frac{1}{\omega C} - \frac{2}{\omega C}}{R} = \tan(-30.9^\circ)$$

$$\frac{\frac{\mathcal{E}}{i} - \frac{1}{\omega C}}{R} = \tan(-30.9^\circ)$$

$$\frac{\mathcal{E}}{i} - \frac{1}{\omega C} = R \tan(-30.9^\circ) \Rightarrow C = \frac{1}{\omega \left(\frac{\mathcal{E}}{i} - R \tan(-30.9^\circ) \right)} = \frac{1}{2\pi(60) \left(\frac{12}{447 \times 10^{-3}} - R \tan(-30.9^\circ) \right)}$$

$$= \underline{\underline{30.55699886 \mu\text{F}}} \quad \text{--- (1')}$$

(3) ← (1')

$$L = \frac{\frac{\mathcal{E}}{i} + \frac{1}{\omega C}}{\omega} = \frac{\frac{12}{447 \times 10^{-3}} + \frac{1}{2\pi(60)C}}{2\pi(60)} = \underline{\underline{301.474806 \text{ mH}}}$$

#46

$$E_m = 220 \text{ V}$$

$$\nu = 400 \text{ Hz}$$

$$R = 220 \ \Omega$$

$$L = 150 \times 10^{-3} \text{ H}$$

$$C = 24 \times 10^{-6} \text{ F}$$

a) $X_C = \frac{1}{\omega C} = \underline{\underline{16.57863991 \ \Omega}}$

b) $Z = \sqrt{R^2 + (X_L - X_C)^2}$
 $= \sqrt{220^2 + (2\pi(400) \cdot 150 \times 10^{-3} - 16.5786\dots)^2}$
Notice: $X_L > X_C$
 $= \underline{\underline{422.2524774 \ \Omega}}$

c) $i_{\text{max}} = \frac{E_m}{Z} = \underline{\underline{0.5210152972 \text{ amp}}}$

d) $C_{\text{eq}} = \frac{1}{\frac{1}{C} + \frac{1}{C}} = \underline{\underline{12 \ \mu\text{F}}}$

e)

C_{eq} is a half of the original


$\rightarrow X_C = \frac{1}{\omega C} \rightarrow \underline{\underline{\text{Doubled}}}$

\rightarrow Since $X_L > X_C$ before, $(X_L - X_C)$ is less, then $Z = \sqrt{R^2 + (X_L - X_C)^2}$ is less.

$\rightarrow \underline{\underline{Z \text{ should decrease}}}$

\rightarrow then $\underline{\underline{i \text{ should increase}}}$

#49

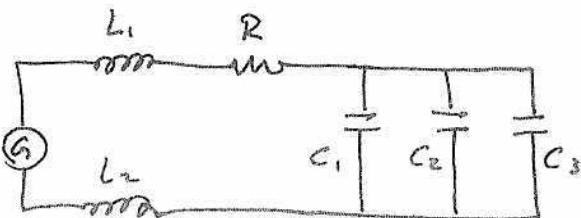

$$R = 100 \ \Omega$$


$$L_1 = 1.7 \times 10^{-3} \text{ H}$$

$$L_2 = 2.3 \times 10^{-3} \text{ H}$$

$$C_1 = 4 \times 10^{-6} \text{ F}$$

$$C_2 = 2.5 \times 10^{-6} \text{ F}$$

$$C_3 = 3.5 \times 10^{-6} \text{ F}$$

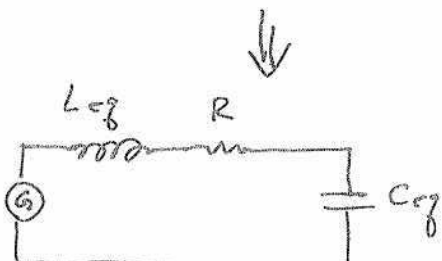

$$(a) C_{eq} = L_1 + L_2 \text{ (Series)} = 4 \times 10^{-3} \text{ H}$$

$$C_{eq} = C_1 + C_2 + C_3 \text{ (parallel)} = 10 \times 10^{-6} \text{ F}$$

$$\omega = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{4 \times 10^{-3} \cdot 10 \times 10^{-6}}} = 5000 \text{ rad/sec}$$


$$\omega = 2\pi\nu \rightarrow \nu = \frac{\omega}{2\pi} = \frac{5000}{2\pi} = \underline{\underline{795.7747155 \text{ Hz}}}$$

(b) Since $\omega_R = \sqrt{\frac{1}{LC}}$ is independent from R, resonant freq. will not change.

(c) If L_1 increases, ω_R decreases \rightarrow ν_{res} also decreases.

(d) If C_3 is gone, C_{eq} decreases \rightarrow ω_R increases & ν_{res} increases

#56

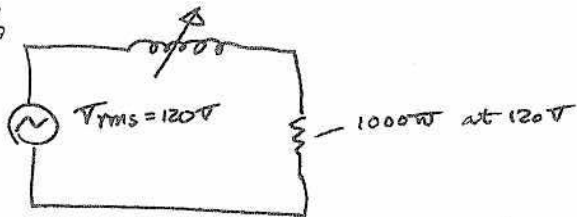

$$V = IR \rightarrow I = \frac{V}{R}$$

$$P = I \cdot V$$

$$\rightarrow P = \frac{V^2}{R} \therefore R = \frac{V^2}{P}$$

$$= \frac{(120)^2}{1000}$$

$$= \underline{\underline{14.4 \Omega}}$$

$$(a) \frac{P_{max}}{P_{min}} = 5 = \frac{V_{max}^2 R}{V_{min}^2 R} = \frac{\left(\frac{V_{rms}}{Z_{min}}\right)^2 \cdot R}{\left(\frac{V_{rms}}{Z_{max}}\right)^2 \cdot R} = \frac{Z_{max}^2}{Z_{min}^2} = \frac{R^2 + (\omega L)^2}{R^2}$$

$$\therefore 5R^2 = R^2 + (\omega L)^2$$

$$L^2 = \frac{4R^2}{\omega^2} = \frac{4R^2}{(2\pi\nu)^2} = \frac{4(14.4)^2}{4\pi^2 \cdot 60^2} = \underline{\underline{7.639437268 \times 10^{-2} \text{ H}}}$$

(b), (c)

modify,ing $5 = \frac{R_{right}^2 + (\omega L)^2}{R^2}$ from (a)

$$5 = \frac{(R_{right} + R)^2}{R_{left}^2}$$


$$5R_{left}^2 = (R_{right} + R)^2$$

$$\sqrt{5} R_{left} = R_{right} + R$$

$$\therefore R = (\sqrt{5}-1) R_{L_{\text{opt}}}$$

$$= (\sqrt{5}-1) (14.4) = \underline{\underline{17.79937888 \Omega}} \quad \text{yes, it can be done}$$

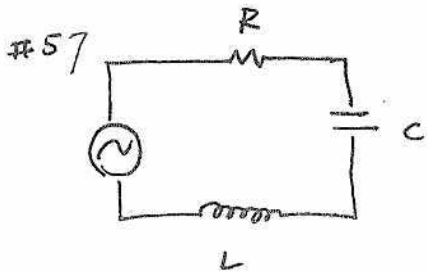- (d) In (a), L stores energy as magnetic energy (which is retractable)
 In (b), R uses energy and it can not be retracted.



$$R = 5 \Omega$$

$$L = 60 \times 10^{-3} \text{ H}$$

$$f_d = 60 \text{ Hz}$$

$$E_m = 30 \text{ V}$$

$$i_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

(a)
$$\overline{P} = (i_{\text{rms}})^2 \cdot R$$

We need to minimize Z , $\rightarrow \sqrt{R^2 + (X_L - X_C)^2}$ minimized.

$$\rightarrow X_L - X_C = 0 \rightarrow \omega L - \frac{1}{\omega C} = 0$$

$$\therefore C = \frac{1}{\omega^2 L} = \frac{1}{(2\pi f)^2 \cdot L} = \underline{\underline{1.172698885 \times 10^{-4} \text{ F}}}$$

- (b) To minimize P , i should be minimized $\rightarrow Z = \infty$. $\rightarrow X_C \rightarrow \infty$
 $\rightarrow \frac{1}{\omega C} = \infty \rightarrow \underline{\underline{C=0}}$

(c)
$$P_{\text{max}} = (i_{\text{max}})^2 \cdot R \quad (\text{when } Z \text{ is minimum})$$

$$= \left(\frac{V_{\text{max}} \sqrt{2}}{R} \right)^2 \cdot R = \frac{V_{\text{max}}^2}{2R} = \underline{\underline{90 \text{ W}}}$$

(f)
$$P_{\text{min}} = 0 \cdot R = \underline{\underline{0 \text{ W}}}$$

P_{max} happens when $i = i_{\text{max}}$.


- (d) i_{max} happens when Z is min $\rightarrow X_L - X_C = 0 \Rightarrow \tan^{-1} \frac{X_L - X_C}{R} = \underline{\underline{0}}$
 (No shift!)

P_{min} happens when $i = 0$

- (g) $i = 0$ when Z is $\infty \rightarrow X_L - X_C = -\infty \rightarrow \tan^{-1} \frac{X_L - X_C}{R} = \underline{\underline{-\frac{\pi}{2}}}$
 (because $C=0$)

- (e) Power factor : $\cos \phi = 1$ for max (I & V are in sync.)
 h) $\cos \phi = 0$ for min (I & V are totally off-sync.)

#59

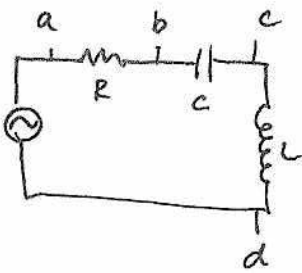

$$R = 15 \Omega$$

$$C = 4.7 \times 10^{-6} \text{ F}$$

$$L = 25 \times 10^{-3} \text{ H}$$

$$V_{\text{rms}} = 75 \text{ V}$$

$$\nu = 550 \text{ Hz} \Rightarrow \omega = 2\pi\nu$$

(a)
$$i_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

$$= \frac{V_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{V_{\text{rms}}}{\sqrt{R^2 + (2\pi\nu L - \frac{1}{2\pi\nu C})^2}} = \underline{\underline{2.585763724 \text{ amp}}}$$

(b)
$$V_{ab \text{ rms}} = iR = \underline{\underline{38.78645587 \text{ V}}}$$

$$V_{bc \text{ rms}} = iX_C = i\left(\frac{1}{\omega C}\right) = \underline{\underline{159.20197646 \text{ V}}}$$

$$V_{cd \text{ rms}} = iX_L = i\omega L = \underline{\underline{223.3939488 \text{ V}}}$$

$$V_{ad \text{ rms}} = V_{\text{rms}} = 75 \text{ V}$$


the difference between rms & #42 is either average (rms) or at any given instance. Make sure you can do both.

(c)
$$P_R = i^2 R = 100.2926106 \text{ W}$$

$$P_C = 0$$

$$P_L = 0 \quad \left. \vphantom{P_C} \right\} \text{ they store energy, they do not disipate energy.}$$

#98

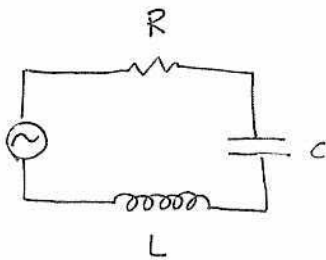

$$R = 200 \Omega$$

$$C = 15 \mu\text{F}$$

$$L = 230 \text{ mH}$$

$$f_d = 60 \text{ Hz}$$

$$E_m = 36.0 \text{ V}$$

(a)
$$E_{\text{max}} = 36.0 \text{ V} \quad (\text{Given})$$

Before we solve for the rest, we need some um L

$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= 219.3708587 \Omega \end{aligned}$$


$$X_L = \omega L = 2\pi \nu L = 87.70775724 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \nu C} = 176.8388257 \Omega$$

$$\therefore i_{\max} = \frac{E_{\max}}{Z} = 0.1641056624 \text{ amp}$$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R} = -24.25891527$$

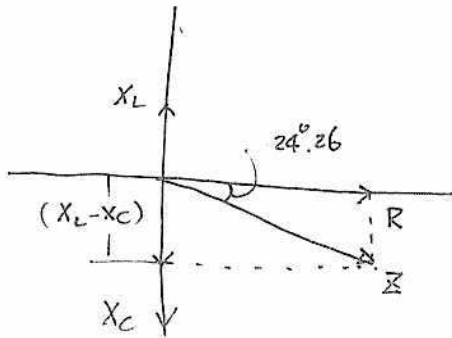Here is the key point to understand LCR circuit.




It's very important to draw a phasor diagram as accurately as possible.

This diagram shows that

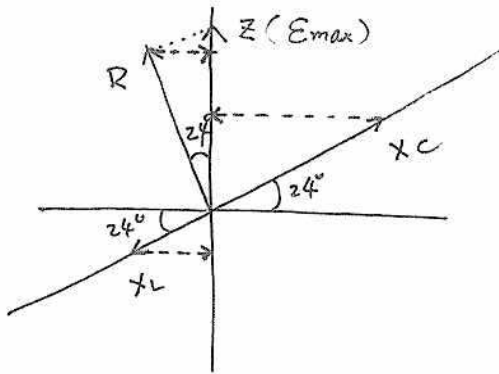1. the current (same direction as R) is 24.26 ahead of V (same direction as Z)
2. y -projections show values of what we are looking for. (In this instant, $i=0$ and $V_{\text{net}} = \text{negative}$, $V_L = i^{\text{th}} \text{max}$, $V_C = i^{\text{th}} \text{min}$, and $V_R = 0$.)

the given condition is that $E = \text{max}$.



So E direction is on y axis and others follow.

At this moment V across each part is

1. Calculate V_{max} of each.
2. project that value on to the y -axis.

Remember that \vec{R} , \vec{X}_C & \vec{X}_L are always rotating. these solutions are true only when $E = E_{\max}$ (when \vec{E} is on y axis)

$$(b) \quad V_R = i_{\max} R \cos 24^\circ \dots = 29.92296485 \text{ V}$$

$$(c) \quad V_C = i_{\max} X_C \sin 24^\circ \dots = 11.9238192 \text{ V}$$

$$(d) \quad V_L = i_{\max} X_L (-\sin 24^\circ) = -5.913671321 \text{ V} \text{ (see the diagram, } V_L \text{ is down)}$$

(e)

$$+ \frac{\quad}{\quad} = 35.93311473 \text{ V} \approx \underline{\underline{36 \text{ V}}}$$