

# HOMEWORK SET 1

**DUE DATE: 1/28/16**

**TEXTBOOK PROBLEMS:**

1.7, 1.14

2.3, 2.7, 2.15, 2.22, 2.34, 2.55

3.17, 3.23, 3.43, 3.48, 3.60

**SUPPLEMENTAL QUESTION:**

Solve the circuit below for the Current(s) and Voltage  $V_{ab}$

