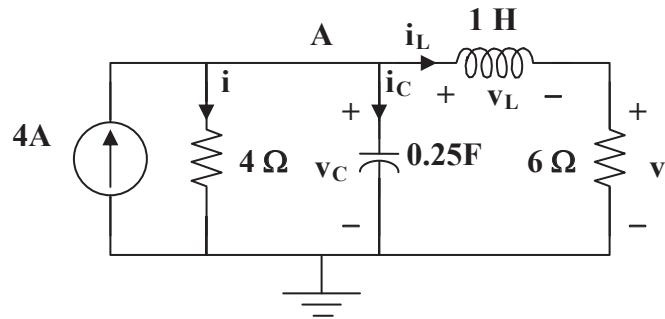


Chapter 8, Solution 5.

(a) For $t < 0$, $4u(t) = 0$ so that the circuit is not active (all initial conditions = 0).

$$i_L(0-) = 0 \text{ and } v_C(0-) = 0.$$

For $t = 0+$, $4u(t) = 4$. Consider the circuit below.



Since the 4-ohm resistor is in parallel with the capacitor,

$$i(0+) = v_C(0+)/4 = 0/4 = 0 \text{ A}$$

Also, since the 6-ohm resistor is in series with the inductor,
 $v(0+) = 6i_L(0+) = 0 \text{ V}.$

$$\begin{aligned} (b) \quad di(0+)/dt &= d(v_R(0+)/R)/dt = (1/R)dv_R(0+)/dt = (1/R)dv_C(0+)/dt \\ &= (1/4)4/0.25 \text{ A/s} = 4 \text{ A/s} \end{aligned}$$

$$v = 6i_L \text{ or } dv/dt = 6di_L/dt \text{ and } dv(0+)/dt = 6di_L(0+)/dt = 6v_L(0+)/L = 0$$

$$\text{Therefore } dv(0+)/dt = 0 \text{ V/s}$$


(c) As t approaches infinity, the circuit is in steady-state.

$$i(\infty) = 6(4)/10 = 2.4 \text{ A}$$

$$v(\infty) = 6(4 - 2.4) = 9.6 \text{ V}$$

Chapter 8, Solution 20.

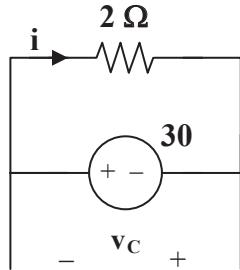For $t < 0$, the equivalent circuit is as shown below.



$$v(0) = -30 \text{ V} \text{ and } i(0) = 30/2 = 15 \text{ A}$$

For $t > 0$, we have a series RLC circuit.

$$\alpha = R/(2L) = 2/(2 \times 0.5) = 2$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{0.5 \times 1/4} = 2\sqrt{2}$$

Since α is less than ω_0 , we have an under-damped response.

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{8 - 4} = 2$$

$$i(t) = (A\cos(2t) + B\sin(2t))e^{-2t}$$

$$i(0) = 15 = A$$


$$di/dt = -2(15\cos(2t) + B\sin(2t))e^{-2t} + (-2 \times 15\sin(2t) + 2B\cos(2t))e^{-2t}$$

$$di(0)/dt = -30 + 2B = -(1/L)[Ri(0) + v_C(0)] = -2[30 - 30] = 0$$

$$\text{Thus, } B = 15 \text{ and } i(t) = (15\cos(2t) + 15\sin(2t))e^{-2t} \text{ A}$$

Chapter 8, Solution 39.

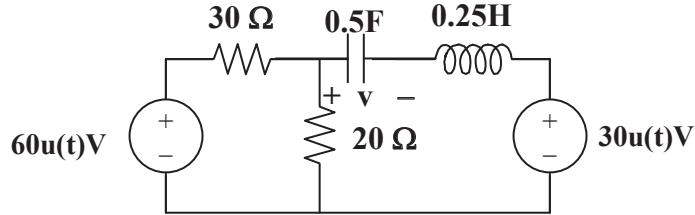For $t = 0^-$, the source voltages are equal to zero thus, the initial conditions are $v(0) = 0$ and $i_L(0) = 0$.



For $t > 0$, the circuit is shown above.

$$R = 20 \parallel 30 = 12 \text{ ohms}$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{(1/2)(1/4)} = \sqrt{8}$$

$$\alpha = R/(2L) = (12)/(0.5) = 24$$

Since $\alpha > \omega_0$, we have an overdamped response.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -47.83, -0.167$$

Thus, $v(t) = V_s + [Ae^{-47.83t} + Be^{-0.167t}]$, where
 $V_s = [60/(30+20)]20 - 30 = -6$ volts.

$$v(0) = 0 = -6 + A + B \text{ or } 6 = A + B \quad (1)$$

$$i(0) = Cdv(0)/dt = 0$$

$$\text{But, } dv(0)/dt = -47.83A - 0.167B = 0 \text{ or}$$

$$B = -286.4A \quad (2)$$

From (1) and (2), $A + (-286.4)A = 6$ or $A = 6/(-285.4) = -0.02102$ and
 $B = -286.4(-0.02102) = 6.02$

$$v(t) = [-6 + (-0.021e^{-47.83t} + 6.02e^{-0.167t})] \text{ volts.}$$

Chapter 8, Solution 43.

For $t > 0$, we have a source-free series RLC circuit.

$$\alpha = \frac{R}{2L} \longrightarrow R = 2\alpha L = 2 \times 8 \times 0.5 = 8\Omega$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 30 \longrightarrow \omega_0 = \sqrt{900 + 64} = \sqrt{964}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega_o^2 L} = \frac{1}{964 \times 0.5} = 2.075 \text{ mF}$$

Chapter 8, Solution 49.

For $t = 0^-$, $i(0) = 3 + 12/4 = 6$ and $v(0) = 0$.

For $t > 0$, we have a parallel RLC circuit with a step input.

$$\alpha = 1/(2RC) = (1)/(2 \times 5 \times 0.05) = 2$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{5 \times 0.05} = 2$$

Since $\alpha = \omega_0$, we have a critically damped response.

$$s_{1,2} = -2$$

Thus, $i(t) = I_s + [(A + Bt)e^{-2t}]$, $I_s = 3$

$$i(0) = 6 = 3 + A \text{ or } A = 3$$

$$v = Ldi/dt \text{ or } v/L = di/dt = [Be^{-2t}] + [-2(A + Bt)e^{-2t}]$$

$$v(0)/L = 0 = di(0)/dt = B - 2x3 \text{ or } B = 6$$

$$\text{Thus, } i(t) = \{3 + [(3 + 6t)e^{-2t}]\} A$$

Chapter 8, Solution 58.

(a) Let i = inductor current, v = capacitor voltage $i(0) = 0$, $v(0) = 4$

$$\frac{dv(0)}{dt} = -\frac{[v(0) + Ri(0)]}{RC} = -\frac{(4 + 0)}{0.5} = -8 \text{ V/s}$$

(b) For $t \geq 0$, the circuit is a source-free RLC parallel circuit.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 0.5 \times 1} = 1, \quad \omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25 \times 1}} = 2$$

$$\omega_d = \sqrt{\omega^2_o - \alpha^2} = \sqrt{4 - 1} = 1.732$$

Thus,

$$v(t) = e^{-t} (A_1 \cos 1.732t + A_2 \sin 1.732t)$$

$$v(0) = 4 = A_1$$

$$\frac{dv}{dt} = -e^{-t} A_1 \cos 1.732t - 1.732e^{-t} A_1 \sin 1.732t - e^{-t} A_2 \sin 1.732t + 1.732e^{-t} A_2 \cos 1.732t$$

$$\frac{dv(0)}{dt} = -8 = -A_1 + 1.732A_2 \quad \longrightarrow \quad A_2 = -2.309$$

$$v(t) = \underline{e^{-t} (4 \cos 1.732t - 2.309 \sin 1.732t) \text{ V}}$$

Chapter 8, Solution 60.

$$\text{At } t = 0, \ 4u(t) = 0 \text{ so that } i_1(0) = 0 = i_2(0) \quad (1)$$

Applying nodal analysis,

$$4 = 0.5di_1/dt + i_1 + i_2 \quad (2)$$

$$\text{Also, } i_2 = [1di_1/dt - 1di_2/dt]/3 \text{ or } 3i_2 = di_1/dt - di_2/dt \quad (3)$$

$$\text{Taking the derivative of (2), } 0 = d^2i_1/dt^2 + 2di_1/dt + 2di_2/dt \quad (4)$$

$$\text{From (2) and (3), } di_2/dt = di_1/dt - 3i_2 = di_1/dt - 3(4 - i_1 - 0.5di_1/dt)$$

$$= di_1/dt - 12 + 3i_1 + 1.5di_1/dt$$

Substituting this into (4),

$$d^2i_1/dt^2 + 7di_1/dt + 6i_1 = 24 \text{ which gives } s^2 + 7s + 6 = 0 = (s + 1)(s + 6)$$

$$\text{Thus, } i_1(t) = I_s + [Ae^{-t} + Be^{-6t}], \ 6I_s = 24 \text{ or } I_s = 4$$

$$i_1(t) = 4 + [Ae^{-t} + Be^{-6t}] \text{ and } i_1(0) = 4 + [A + B] \quad (5)$$

$$i_2 = 4 - i_1 - 0.5di_1/dt = i_1(t) = 4 + -4 - [Ae^{-t} + Be^{-6t}] - [-Ae^{-t} - 6Be^{-6t}]$$

$$= [-0.5Ae^{-t} + 2Be^{-6t}] \text{ and } i_2(0) = 0 = -0.5A + 2B \quad (6)$$

$$\text{From (5) and (6), } A = -3.2 \text{ and } B = -0.8$$

$$i_1(t) = \{4 + [-3.2e^{-t} - 0.8e^{-6t}]\} A$$

$$i_2(t) = [1.6e^{-t} - 1.6e^{-6t}] A$$

Chapter 8, Solution 63.


$$\frac{v_s - 0}{R} = C \frac{d(0 - v_o)}{dt} \quad \longrightarrow \quad \frac{v_s}{R} = -C \frac{dv_o}{dt}$$
$$v_o = L \frac{di}{dt} \quad \longrightarrow \quad \frac{dv_o}{dt} = L \frac{d^2i}{dt^2} = -\frac{v_s}{RC}$$

Thus,

$$\frac{d^2i(t)}{dt^2} = -\frac{v_s}{RCL}$$

Chapter 8, Solution 66.

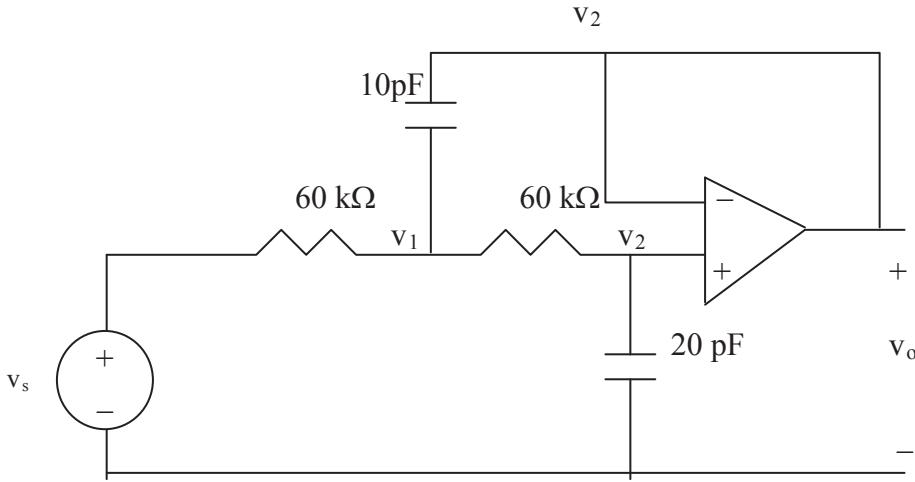We apply nodal analysis to the circuit as shown below.



At node 1,

$$\frac{v_s - v_1}{60k} = \frac{v_1 - v_2}{60k} + 10pF \frac{d}{dt}(v_1 - v_o)$$

But $v_2 = v_o$

$$v_s = 2v_1 - v_o + 6 \times 10^{-7} \frac{d(v_1 - v_o)}{dt} \quad (1)$$

At node 2,

$$\frac{v_1 - v_2}{60k} = 20pF \frac{d}{dt}(v_2 - 0), \quad v_2 = v_o$$

$$v_1 = v_o + 1.2 \times 10^{-6} \frac{dv_o}{dt} \quad (2)$$

Substituting (2) into (1) gives

$$v_s = 2 \left(v_o + 1.2 \times 10^{-6} \frac{dv_o}{dt} \right) - v_o + 6 \times 10^{-7} \left(1.2 \times 10^{-6} \frac{d^2 v_o}{dt^2} \right)$$

$$v_s = v_o + 2.4 \times 10^{-6} (dv_o/dt) + 7.2 \times 10^{-13} (d^2 v_o / dt^2).$$

Chapter 9, Solution 2.

(a) amplitude = **15 A**

(b) $\omega = 25\pi = \mathbf{78.54 \text{ rad/s}}$

(c) $f = \frac{\omega}{2\pi} = \mathbf{12.5 \text{ Hz}}$

(d) $I_s = 15\angle 25^\circ \text{ A}$
 $I_s(2 \text{ ms}) = 15 \cos((500\pi)(2 \times 10^{-3}) + 25^\circ)$
= $15 \cos(\pi + 25^\circ) = 15 \cos(205^\circ)$
= **-13.595 A**

Chapter 9, Solution 8.

$$\begin{aligned}
 (a) \quad & \frac{60\angle 45^\circ}{7.5 - j10} + j2 = \frac{60\angle 45^\circ}{12.5\angle -53.13^\circ} + j2 \\
 &= 4.8\angle 98.13^\circ + j2 = -0.6788 + j4.752 + j2 \\
 &= \mathbf{-0.6788 + j6.752}
 \end{aligned}$$

$$(b) \quad (6-j8)(4+j2) = 24-j32+j12+16 = 40-j20 = 44.72\angle -26.57^\circ$$

$$\begin{aligned}
 & \frac{32\angle -20^\circ}{(6-j8)(4+j2)} + \frac{20}{-10+j24} = \frac{32\angle -20^\circ}{44.72\angle -26.57^\circ} + \frac{20}{26\angle 112.62^\circ} \\
 &= 0.7156\angle 6.57^\circ + 0.7692\angle -112.62^\circ = 0.7109 + j0.08188 - 0.2958 - j0.71 \\
 &= \mathbf{0.4151 - j0.6281}
 \end{aligned}$$

$$\begin{aligned}
 (c) \quad & 20 + (16\angle -50^\circ)(13\angle 67.38^\circ) = 20 + 208\angle 17.38^\circ = 20 + 198.5 + j62.13 \\
 &= \mathbf{218.5 + j62.13}
 \end{aligned}$$

Chapter 9, Solution 31.

$$L = 240mH \quad \longrightarrow \quad j\omega L = j2x240x10^{-3} = j0.48$$

$$C = 5mF \quad \longrightarrow \quad \frac{1}{j\omega C} = \frac{1}{j2x5x10^{-3}} = -j100$$

$$Z = 80 + j0.48 - j100 = 80 - j99.52 =$$

$$I = \frac{V}{Z} = \frac{10 < 0^\circ}{80 - j99.52} = 0.0783 < 51.206^\circ$$

$$i(t) = 78.3 \cos(2t + 51.21^\circ) \text{ mA}$$

Chapter 9, Solution 37.

$$Y = (1/4) + (1/(j8)) + (1/(-j10)) = 0.25 - j0.025$$

$$= (250-j25) \text{ mS}$$

Chapter 9, Solution 39.

$$Z_{eq} = 4 + j20 + 10 // (-j14 + j25) = \underline{9.135 + j27.47 \Omega}$$

$$= (9.135 + j27.47) \Omega$$

$$I = \frac{V}{Z_{eq}} = \frac{12}{9.135 + j27.47} = 0.4145 < -71.605^\circ$$

$$i(t) = 414.5 \cos(10t - 71.6^\circ) \text{ mA}$$


Chapter 9, Solution 60.

$$Z = (25 + j15) + (20 - j50) // (30 + j10) = 25 + j15 + 26.097 - j5.122$$

$$Z = (51.1 + j9.878) \Omega$$

Supplemental Question

MODEL:

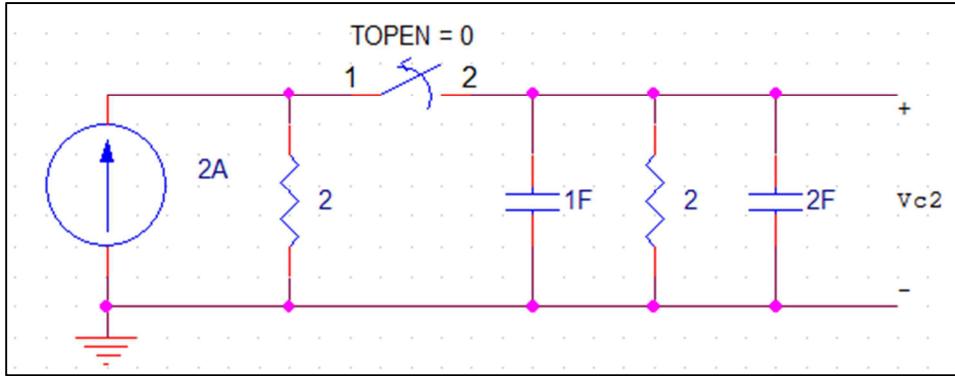

- a. Determine the equation that represents "Vc2"

INITIAL CONDITIONS

$$Vc(0-) = Vc(0+) = 2V$$

$$Vc(\infty) = 0V$$

CIRCUIT EQUATION

$$C1 \frac{dVc}{dt} + Vc / R + C2 \frac{dVc}{dt} = 0$$

$$\frac{dVc}{dt} (C1 + C2) + Vc/2 = 0$$

$$\tau = (C1 + C2) * R = 6 \text{ Seconds}$$

GENERAL SOLUTION

$$Vc(t) = Vh + Vp$$

$$Vh = Ke^{-t/\tau}$$

$$Vc(0+) = 2 = Ke^0 + Vp$$

$$\rightarrow K = 2 - Vp$$

$$Vp = Vc(\infty) = 0$$

$$Vc(t) = 2e^{-t/\tau}$$

- b. Sketch the voltage characteristics

Transient Response

