

### Chapter 11, Solution 7.

Applying KVL to the left-hand side of the circuit,

$$8\angle 20^\circ = 4\mathbf{I}_o + 0.1\mathbf{V}_o \quad (1)$$

Applying KCL to the right side of the circuit,

$$8\mathbf{I}_o + \frac{\mathbf{V}_1}{j5} + \frac{\mathbf{V}_1}{10 - j5} = 0$$

But, 
$$\mathbf{V}_o = \frac{10}{10 - j5}\mathbf{V}_1 \longrightarrow \mathbf{V}_1 = \frac{10 - j5}{10}\mathbf{V}_o$$

Hence, 
$$8\mathbf{I}_o + \frac{10 - j5}{j50}\mathbf{V}_o + \frac{\mathbf{V}_o}{10} = 0$$

$$\mathbf{I}_o = j0.025\mathbf{V}_o \quad (2)$$

Substituting (2) into (1),

$$8\angle 20^\circ = 0.1\mathbf{V}_o(1 + j)$$


$$\mathbf{V}_o = \frac{80\angle 20^\circ}{1 + j}$$

$$\mathbf{I}_1 = \frac{\mathbf{V}_o}{10} = \frac{8}{\sqrt{2}}\angle -25^\circ$$

$$P = \frac{1}{2}|\mathbf{I}_1|^2 R = \left(\frac{1}{2}\right)\left(\frac{64}{2}\right)(10) = \mathbf{160W}$$
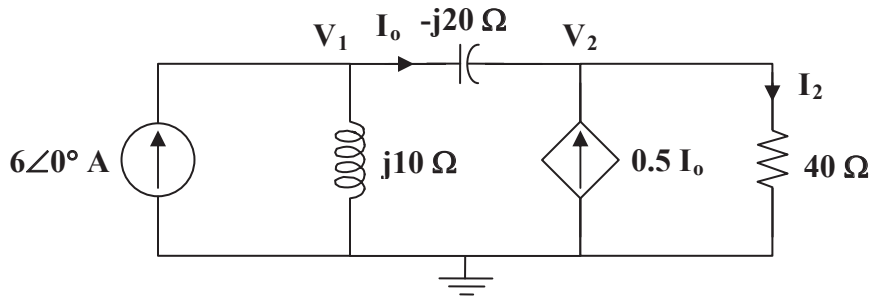
### Chapter 11, Solution 8.

We apply nodal analysis to the following circuit.



At node 1,

$$6 = \frac{V_1}{j10} + \frac{V_1 - V_2}{-j20} \quad V_1 = j120 - V_2 \quad (1)$$

At node 2,

$$0.5 I_o + I_o = \frac{V_2}{40}$$

But, 
$$I_o = \frac{V_1 - V_2}{-j20}$$

Hence, 
$$\frac{1.5(V_1 - V_2)}{-j20} = \frac{V_2}{40}$$

$$3V_1 = (3 - j)V_2 \quad (2)$$

Substituting (1) into (2),

$$j360 - 3V_2 - 3V_2 + jV_2 = 0$$


$$V_2 = \frac{j360}{6 - j} = \frac{360}{37}(-1 + j6)$$

$$I_2 = \frac{V_2}{40} = \frac{9}{37}(-1 + j6)$$

$$P = \frac{1}{2} |I_2|^2 R = \frac{1}{2} \left( \frac{9}{\sqrt{37}} \right)^2 (40) = 43.78 \text{ W}$$

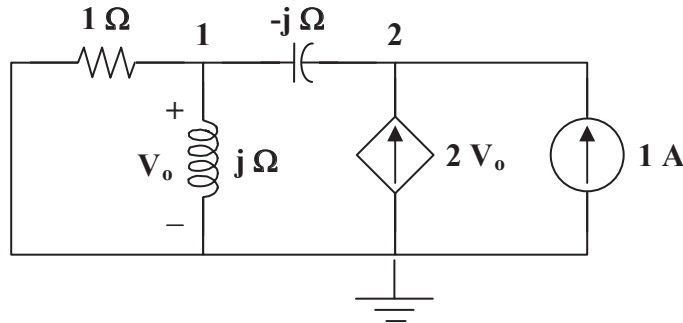**Chapter 11, Solution 15.**

To find  $Z_{eq}$ , insert a 1-A current source at the load terminals as shown in Fig. (a).



(a)

At node 1,

$$\frac{V_o}{1} + \frac{V_o}{j} = \frac{V_2 - V_o}{-j} \longrightarrow V_o = jV_2 \quad (1)$$

At node 2,

$$1 + 2V_o = \frac{V_2 - V_o}{-j} \longrightarrow 1 = jV_2 - (2 + j)V_o \quad (2)$$

Substituting (1) into (2),


$$1 = jV_2 - (2 + j)(j)V_2 = (1 - j)V_2$$

$$V_2 = \frac{1}{1 - j}$$

$$Z_{eq} = \frac{V_2}{1} = \frac{1 + j}{2} = 0.5 + j0.5$$

$$Z_L = Z_{eq}^* = [0.5 - j0.5] \Omega$$

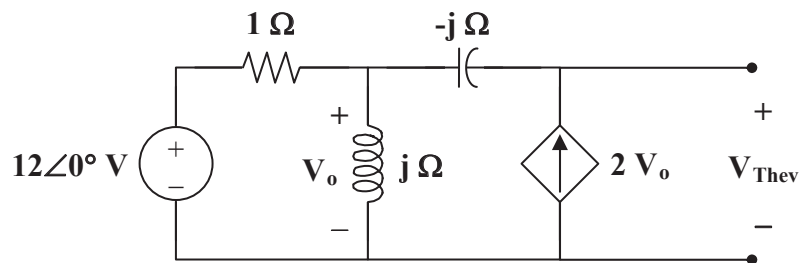We now obtain  $V_{Thev}$  from Fig. (b).



(b)

$$-2V_o + \frac{V_o - 12}{1} + \frac{V_o}{j} = 0$$

$$\mathbf{V}_o = \frac{-12}{1+j}$$

$$-\mathbf{V}_o - (-j \times 2 \mathbf{V}_o) + \mathbf{V}_{Th} = 0$$

$$\mathbf{V}_{Thev} = (1-j2)\mathbf{V}_o = \frac{(-12)(1-j2)}{1+j}$$


$$P_{\max} = \frac{\left[ \frac{V_{Thev}}{0.5 + j0.5 + 0.5 - j0.5} \right]^2}{2} \cdot 0.5 = \frac{\left( \frac{12\sqrt{5}}{\sqrt{2}} \right)^2}{2(2 \times 0.5)^2} \cdot 0.5$$

$$= \mathbf{90 \text{ W}}$$

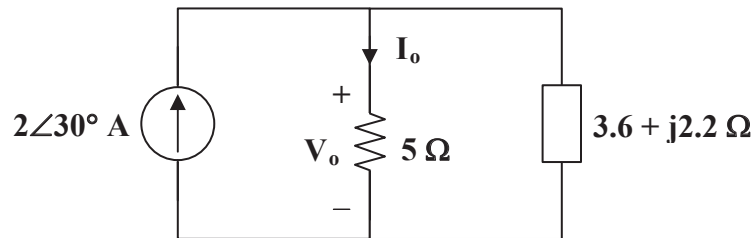**Chapter 11, Solution 56.**

$$-j2 \parallel 6 = \frac{(6)(-j2)}{6-j2} = \frac{12\angle -90^\circ}{6.32456\angle -18.435^\circ} = 1.897365\angle -71.565^\circ = 0.6 - j1.8$$
$$3 + j4 + [(-j2) \parallel 6] = 3.6 + j2.2$$

The circuit is reduced to that shown below.



$$I_o = \frac{3.6 + j2.2}{8.6 + j2.2} (2\angle 30^\circ) = \frac{4.219\angle 31.4296^\circ}{8.87694\angle 14.3493^\circ} (2\angle 30^\circ) = 0.95055\angle 47.08^\circ$$

$$V_o = 5I_o = 4.75275\angle 47.08^\circ$$

$$S = V_o I_s^* = (4.75275\angle 47.08^\circ)(2\angle -30^\circ)$$


$$S = 9.5055\angle 17.08^\circ = \mathbf{(9.086 + j2.792) \text{ VA}}$$

### Chapter 11, Solution 58.

From the left portion of the circuit,

$$\mathbf{I}_o = \frac{0.2}{500} = 0.4 \text{ mA}$$

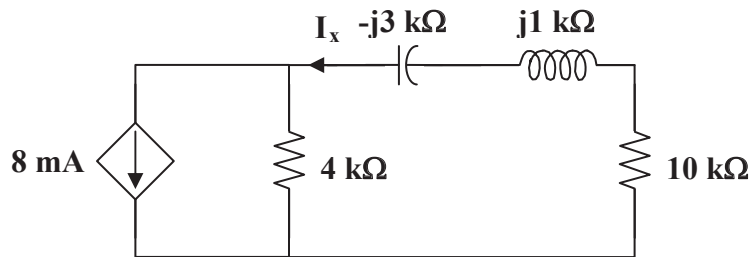$20\mathbf{I}_o = 8 \text{ mA}$  which then leads to the following circuit,



From the right portion of the circuit,

$$\mathbf{I}_x = \frac{4}{4 + 10 + j - j3} (8 \text{ mA}) = \frac{16}{7 - j} \text{ mA}$$


$$\mathbf{S} = |\mathbf{I}_x|^2 \mathbf{R} = \frac{(16 \times 10^{-3})^2}{50} \cdot (10 \times 10^3)$$

$$\mathbf{S} = 51.2 \text{ mVA}$$

It should be noted that the complex power delivered to a resistor is always watts.
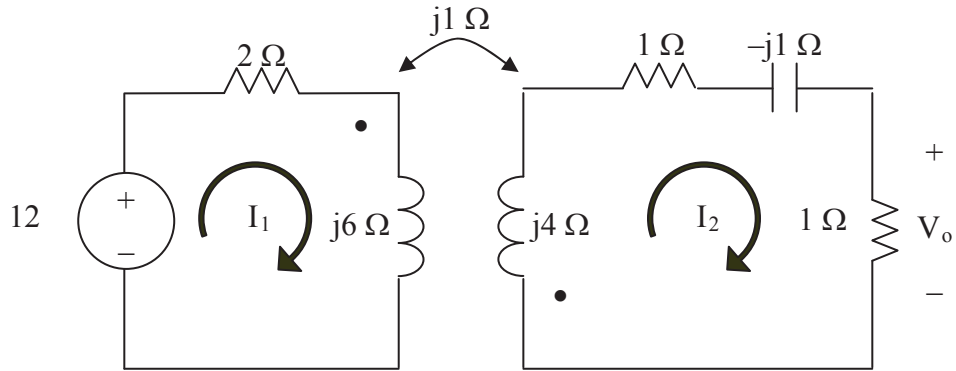
### Chapter 13, Solution 7.

We apply mesh analysis to the circuit as shown below.



For mesh 1,  
 $(2+j6)I_1 + jI_2 = 24$

For mesh 2,  
 $jI_1 + (2-j+j4)I_2 = jI_1 + (2+j3)I_2 = 0$  or  $I_1 = (-3+j2)I_2$

Substituting into the first equation results in  $I_2 = (-0.8762+j0.6328)$  A.

$$V_o = I_2 \times 1 = \mathbf{1.081 \angle 144.16^\circ \text{ V.}}$$

**Chapter 13, Solution 17.**


$$j\omega L = j40 \quad \longrightarrow \quad \omega = \frac{40}{L} = \frac{40}{15 \times 10^{-3}} = 2667 \text{ rad/s}$$

$$M = k\sqrt{L_1 L_2} = 0.6\sqrt{12 \times 10^{-3} \times 30 \times 10^{-3}} = 11.384 \text{ mH}$$

If 15 mH  $\longrightarrow$  40  $\Omega$

Then 12 mH  $\longrightarrow$  32  $\Omega$   
 30 mH  $\longrightarrow$  80  $\Omega$   
 11.384 mH  $\longrightarrow$  30.36  $\Omega$

The circuit becomes that shown below.

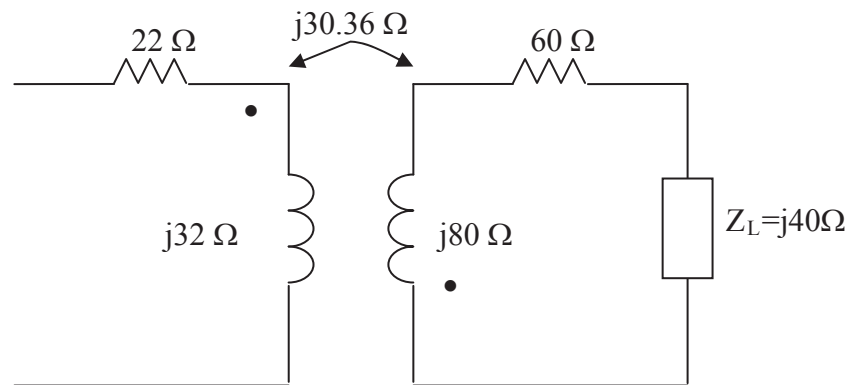

$$\begin{aligned} Z_{in} &= 22 + j32 + \frac{\omega^2 M^2}{j80 + 60 + j40} = 22 + j32 + \frac{(30.36)^2}{60 + j120} \\ &= 22 + j32 + \frac{921.7}{134.16 \angle 63.43^\circ} = 22 + j32 + 6.87 \angle -63.43^\circ = 22 + j32 + 3.073 - j6.144 \\ &= [25.07 + j25.86] \Omega. \end{aligned}$$




**Chapter 13, Solution 27.**

$$1H \longrightarrow j\omega L = j20$$

$$2H \longrightarrow j\omega L = j40$$

$$0.5H \longrightarrow j\omega L = j10$$

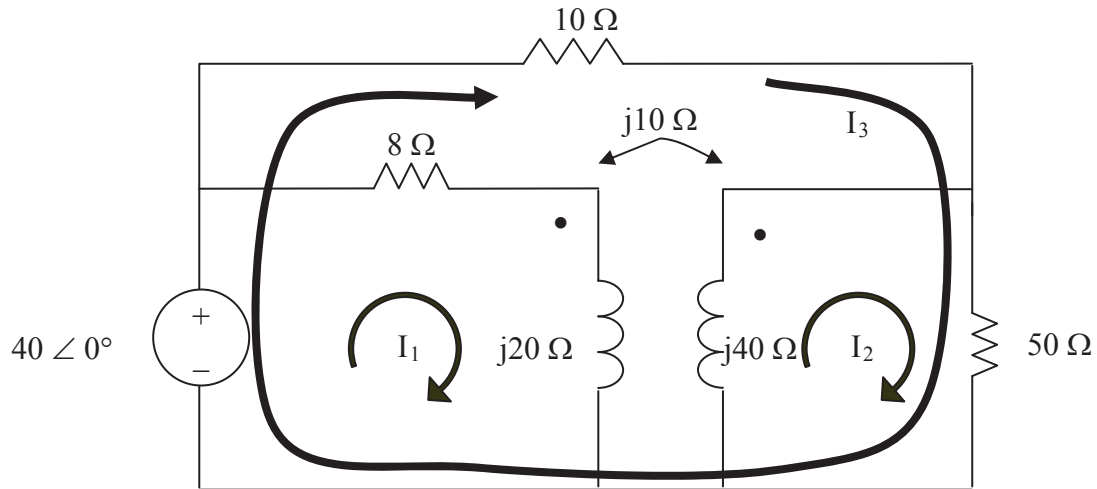We apply mesh analysis to the circuit as shown below.



To make the problem easier to solve, let us have  $I_3$  flow around the outside loop as shown.

For mesh 1,

$$-40 + 8I_1 + j20I_1 - j10I_2 = 0 \text{ or } (8+j20)I_1 - j10I_2 = 40 \quad (1)$$

For mesh 2,

$$j40I_2 - j10I_1 + 50(I_2 + I_3) = 0 \text{ or } -j10I_1 + (50+j40)I_2 + 50I_3 = 0 \quad (2)$$

For mesh 3,

$$-40 + 10I_3 + 50(I_3 + I_2) = 0 \text{ or } 50I_2 + 60I_3 = 40 \quad (3)$$

In matrix form, (1) to (3) become

$$\begin{bmatrix} 8+j20 & -j10 & 0 \\ -j10 & 50+j40 & 50 \\ 0 & 50 & 60 \end{bmatrix} \mathbf{I} = \begin{bmatrix} 40 \\ 0 \\ 40 \end{bmatrix}$$

$$\gg Z = [(8+20i), -10i, 0; -10i, (50+40i), 50; 0, 50, 60]$$

Z =

$$\begin{bmatrix} 8.0000 + 20.0000i & 0 & -10.0000i & 0 \\ 0 & -10.0000i & 50 & 50 \\ 0 & 50 & 60 & 0 \end{bmatrix}$$

$$\begin{array}{cccc} 0 & -10.0000i & 50.0000 & +40.0000i & 50.0000 \\ 0 & 50.0000 & & 60.0000 & \end{array}$$

```
>> V=[40;0;40]
```

```
V =
    40
     0
    40
```

```
>> I=inv(Z)*V
```

```
I =
    0.6354 - 1.5118i
    0.0613 + 0.4682i
    0.6156 - 0.3901i
```

Solving this leads to  $\mathbf{I}_{50} = \mathbf{I}_2 + \mathbf{I}_3 = 0.0613 + 0.6156 + j(0.4682 - 0.3901) =$

$0.6769 + j0.0781 = 0.6814 \angle 6.58^\circ \text{ A}$  or  $\mathbf{I}_{50\text{rms}} \quad |\mathbf{I}_{50\text{rms}}| = 0.6814 / 1.4142 = 481.8 \text{ mA}$ .

The power delivered to the  $50\text{-}\Omega$  resistor is

$$P = (\mathbf{I}_{50\text{rms}})^2 R = (0.4818)^2 50 = \mathbf{11.608 \text{ W}}.$$

**Chapter 13, Solution 36.**

Following the two rules in section 13.5, we obtain the following:

(a)  $V_2/V_1 = -\mathbf{n}, \quad I_2/I_1 = -\mathbf{1/n} \quad (\mathbf{n} = V_2/V_1)$


(b)  $V_2/V_1 = -\mathbf{n}, \quad I_2/I_1 = -\mathbf{1/n}$

(c)  $V_2/V_1 = \mathbf{n}, \quad I_2/I_1 = \mathbf{1/n}$

(d)  $V_2/V_1 = \mathbf{n}, \quad I_2/I_1 = -\mathbf{1/n}$
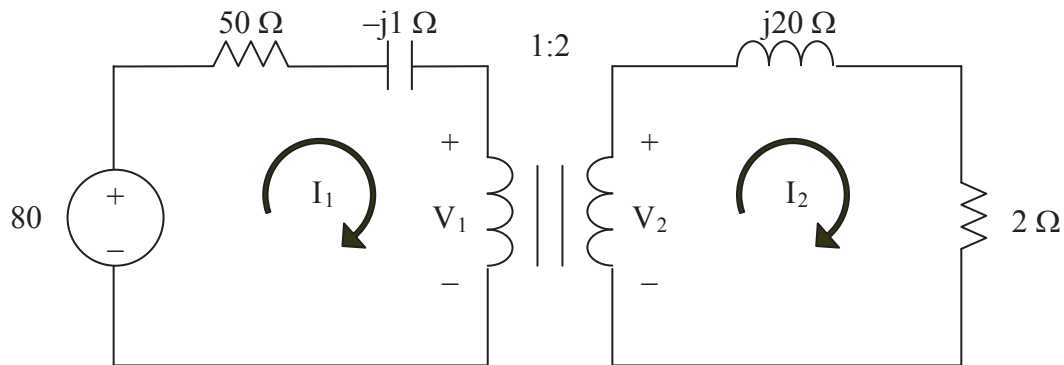
### Chapter 13, Solution 42.

We apply mesh analysis to the circuit as shown below.



For mesh 1,

$$-80 + (50-j)I_1 + V_1 = 0 \quad (1)$$

For mesh 2,

$$-V_2 + (2+j20)I_2 = 0 \quad (2)$$

At the transformer terminals,

$$V_2 = 2V_1 \text{ or } 2V_1 - V_2 = 0 \quad (3)$$

$$I_1 = 2I_2 \text{ or } I_1 - 2I_2 = 0 \quad (4)$$

From (1) to (4),

$$\begin{bmatrix} 50-j & 0 & 1 & 0 \\ 0 & 2+j20 & 0 & -1 \\ 0 & 0 & 2 & -1 \\ 1 & -2 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 80 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solving this with MATLAB,

```
>> A = [(50-j) 0 1 0; 0 (2+20j) 0 -1; 0 0 2 -1; 1 -2 0 0]
```

A =

Columns 1 through 3

```
50.0000 - 1.0000i    0    1.0000
    0    2.0000 + 20.0000i    0
    0    0    2.0000
1.0000    -2.0000    0
```

Column 4

```
0
-1.0000
-1.0000
```

0

```
>> B = [80;0;0;0]
```

B =

```
80  
0  
0  
0
```

```
>> C = inv(A)*B
```

C =

```
1.5743 - 0.1247i      (I1)  
0.7871 - 0.0623i      (I2)  
1.4106 + 7.8091i      (V1)  
2.8212 +15.6181i      (V2)
```

$$I_2 = (787.1 - j62.3) \text{ mA or } 789.6 \angle -4.53^\circ \text{ mA}$$

The power absorbed by the 2- $\Omega$  resistor is

$$P = |I_2|^2 R = (0.7896)^2 2 = \mathbf{1.2469 \text{ W}}$$

**Chapter 13, Solution 57.**

(a)  $Z_L = j3 \parallel (12 - j6) = j3(12 - j6)/(12 - j3) = (12 + j54)/17$

Reflecting this to the primary side gives

$$Z_{in} = 2 + Z_L/n^2 = 2 + (3 + j13.5)/17 = 2.3168 \angle 20.04^\circ$$

$$I_1 = v_s/Z_{in} = 60 \angle 90^\circ / 2.3168 \angle 20.04^\circ = \mathbf{25.9 \angle 69.96^\circ \text{ A(rms)}}$$

$$I_2 = I_1/n = \mathbf{12.95 \angle 69.96^\circ \text{ A(rms)}}$$

(b)  $60 \angle 90^\circ = 2I_1 + v_1$  or  $v_1 = j60 - 2I_1 = j60 - 51.8 \angle 69.96^\circ$

$$v_1 = \mathbf{21.06 \angle 147.44^\circ \text{ V(rms)}}$$

$$v_2 = nv_1 = \mathbf{42.12 \angle 147.44^\circ \text{ V(rms)}}$$

$$v_o = v_2 = \mathbf{42.12 \angle 147.44^\circ \text{ V(rms)}}$$

(c)  $S = v_s I_1^* = (60 \angle 90^\circ)(25.9 \angle -69.96^\circ) = \mathbf{1.554 \angle 20.04^\circ \text{ kVA}}$