


## HOMEWORK SET 9

**TEXTBOOK PROBLEMS:**


None

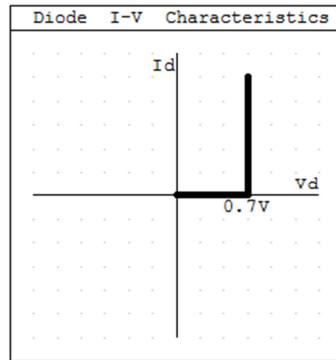**SUPPLEMENTAL QUESTIONS:**


- Given the provided diodes I-V characteristics, determine the following circuit characteristics:



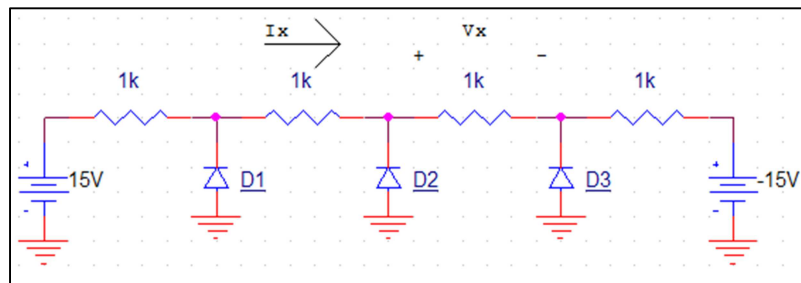
- Find the voltage " $V_x$ " and the current " $I_x$ "



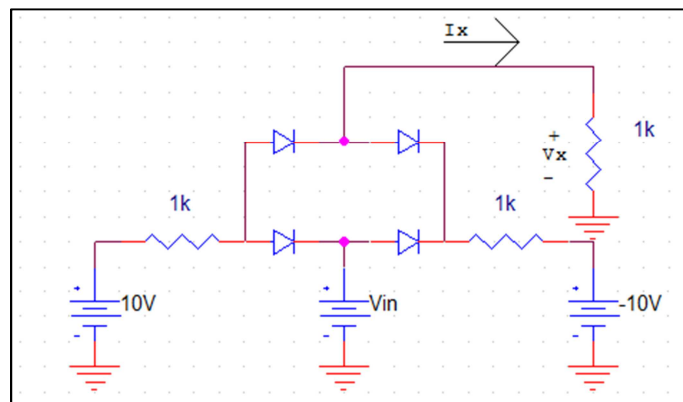
- Plot the voltage " $V_x$ " and the current " $I_x$ " for  $V_{in} = [-10 \text{ to } 10] V$ . It is recommended you use Excel or Matlab to generate the plot in 0.1V increments.



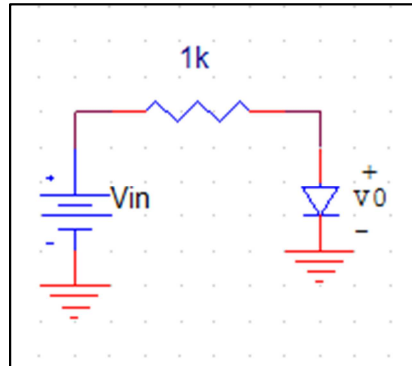2. Consider the circuit show below and answer the following:
  - a. Construct the diodes I-V characteristics assuming the diode represents a physical component with the following specifications [ $T = 300\text{K}$ ,  $I_s = 10^{-14}\text{A}$ ,  $n = 1$ ]
  - b. Construct the load-line behavior of the circuit by finding the points where the diode current [ $I_D = 0$ ] and the diode voltage [ $V_D = 0$ ] given the supply voltage [ $V_{in} = 10\text{VDC}$ ]
  - c. From the chart you have just constructed, determine the quiescent operating point for this circuit
  - d. Now assume that “ $V_{in}$ ” includes an AC source given by: [ $V_{in} = 10 + 0.5\sin(2000 \pi t)$ ], determine the maximum and minimum diode voltage and currents





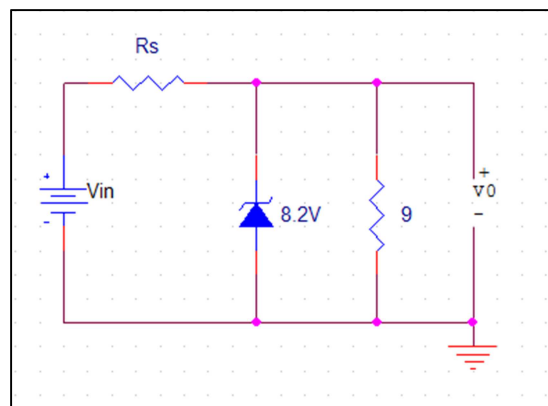3. Consider the voltage regulator circuit shown below. The Zener diode provides a constant reverse bias voltage of [ $V_z = 8.2\text{V}$ ] for  $I_z = [0.75 \text{ to } 1.0]$  A. Select the value of “ $R_s$ ” so that the output voltage [ $V_L = 8.2\text{V}$ ] while the input voltage “ $V_{in}$ ” varies +/- 10% from 12V.





4. Design a clipper circuit to clip off the portions of an input voltage that fall above 3V or below -5V for an input voltage range between -10V to +10V. You may use Schottky diodes that approximate the ideal diode model with a [ $V_f = 0.7\text{V}$ ] and any Zener diode you wish. Supply rails for your circuit are +/- 15V. Ensure that the peak currents through any diode do not exceed 1mA.

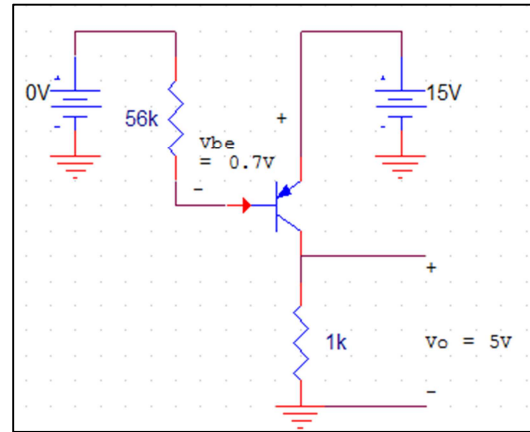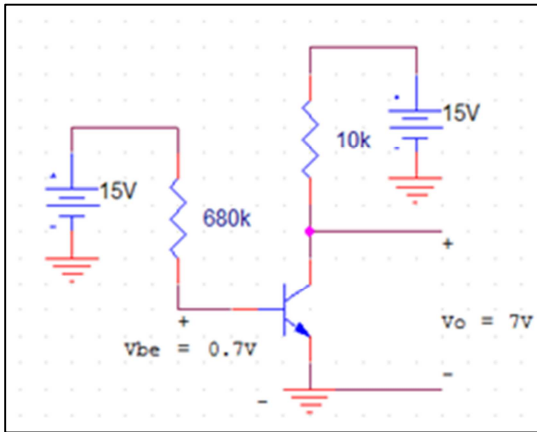
5. Determine both the current gain “ $\beta$ ” and the collector-emitter current ratio “ $\alpha$ ” for the following circuits:



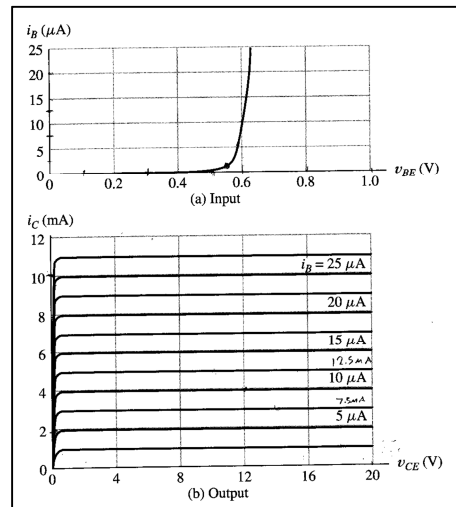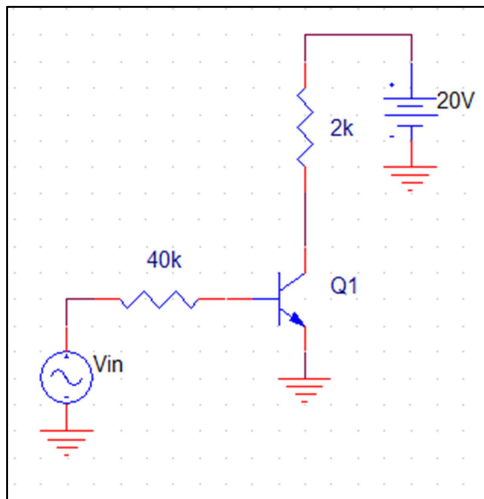
6. Consider the common emitter amplifier shown with a source excitation of  $[V_{in} = 0.8 + 0.2\sin(2000\pi t)]$ . Using the provided operating characteristics of the BJT transistor, answer the following questions:




- Construct the load-line behavior of the amplifier and determine the maximum, minimum and quiescent point (Q-point) for “ $I_b$ ” and “ $V_{be}$ ” and “ $I_c$ ” and “ $V_{ce}$ ”.
  - Draw the “ $V_{in}$ ” and “ $V_{out}$ ” waveforms. You may want to use Matlab or Excel.
7. Consider the common emitter amplifier shown with a source excitation of  $[V_{in} = 8.2 + 0.2\sin(2000\pi t)]$ . The BJT has the following characteristics  $[\beta = 50, I_s = 10^{-13}A]$

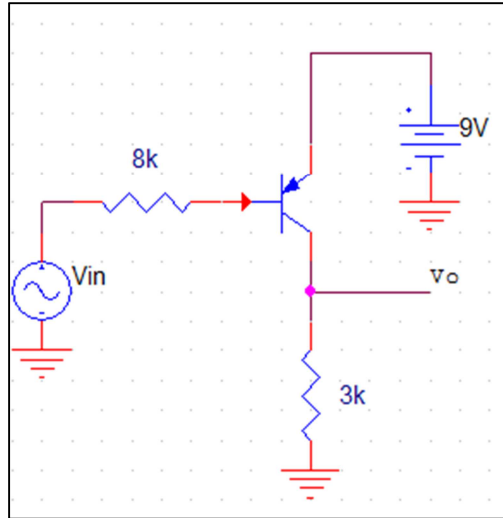

- Construct the load-line behavior of the amplifier and determine the maximum, minimum and quiescent point (Q-point) for " $I_b$ " and " $V_{be}$ " and " $I_c$ " and " $V_o$ ".
  - What is the voltage gain of the amplifier?
  - Draw the " $V_{in}$ " and " $V_{out}$ " waveforms. You may want to use Matlab or Excel.
  - Simulate your results using PSPICE and verify your analysis. Be sure and explain the root cause of any discrepancies.
  - Explain the differences in the signal characteristics from Question-2
8. Consider the common emitter amplifier with negative feedback as shown where the BJT has the following characteristics [ $\beta = 100$ ,  $V_{be} = 0.7V$ ]. If a bias point of [ $V_{ce} = 0.5V$ ] and [ $I_C = 2mA$ ] are required, determine the value of " $R_1$ " and " $R_C$ ".

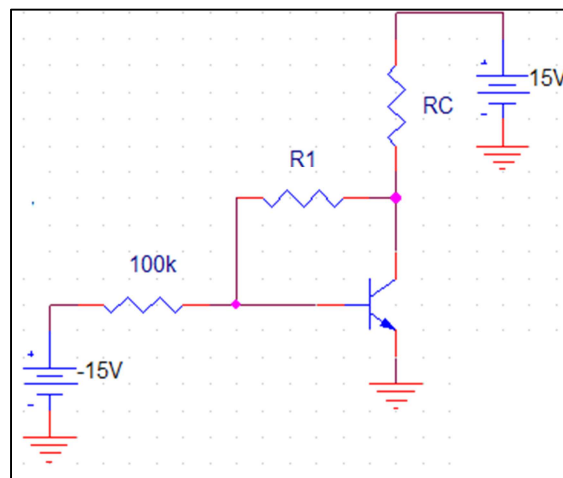

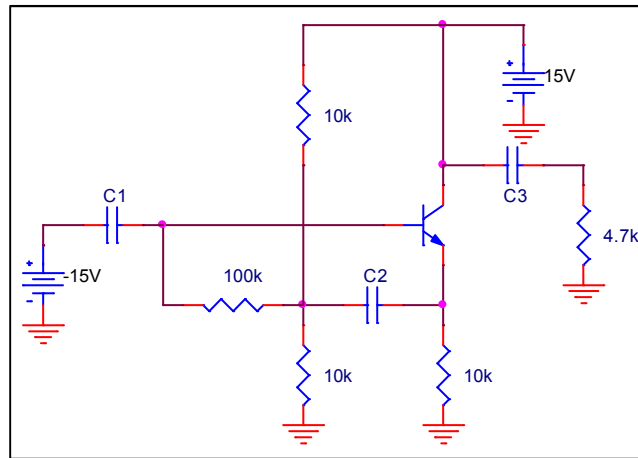9. Consider the amplifier shown below and answer the following questions considering the BJT has the following characteristics [ $\beta = 200$ ,  $V_{beqQ} = 0.7V$ ]. You can assume that each capacitor is sufficiently large to look like an AC short circuit.



- Draw the small-signal equivalent circuit
- Determine the voltage gain
- Determine the input impedance